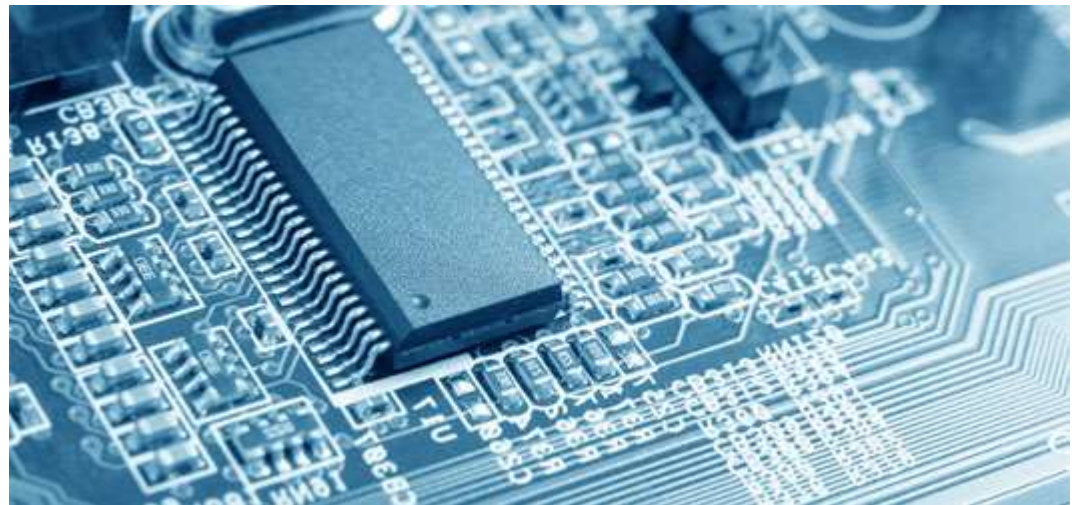




NAZARBAYEV
UNIVERSITY

SCHOOL OF SCIENCE AND TECHNOLOGY



ROBT206 – Microcontrollers with Lab

Lectures 12 – Arithmetic Functions

20 February, 2018

Topics

Today's Topics

Iterative circuits

Binary Adders

- Half and full adders


- Ripple carry and carry look-ahead adders

Binary Subtraction

Iterative Combinational Circuits

- ▶ Arithmetic functions
 - ▶ Operate on binary vectors
 - ▶ Use the same subfunction in each bit position
 - ▶ One can design a **functional block** for the subfunction and **repeat** it to obtain functional block for overall function
 - ▶ *Iterative array* - an array of interconnected cells (1-D or 2-D arrays)
-

Block Diagram of a 1D Iterative Array

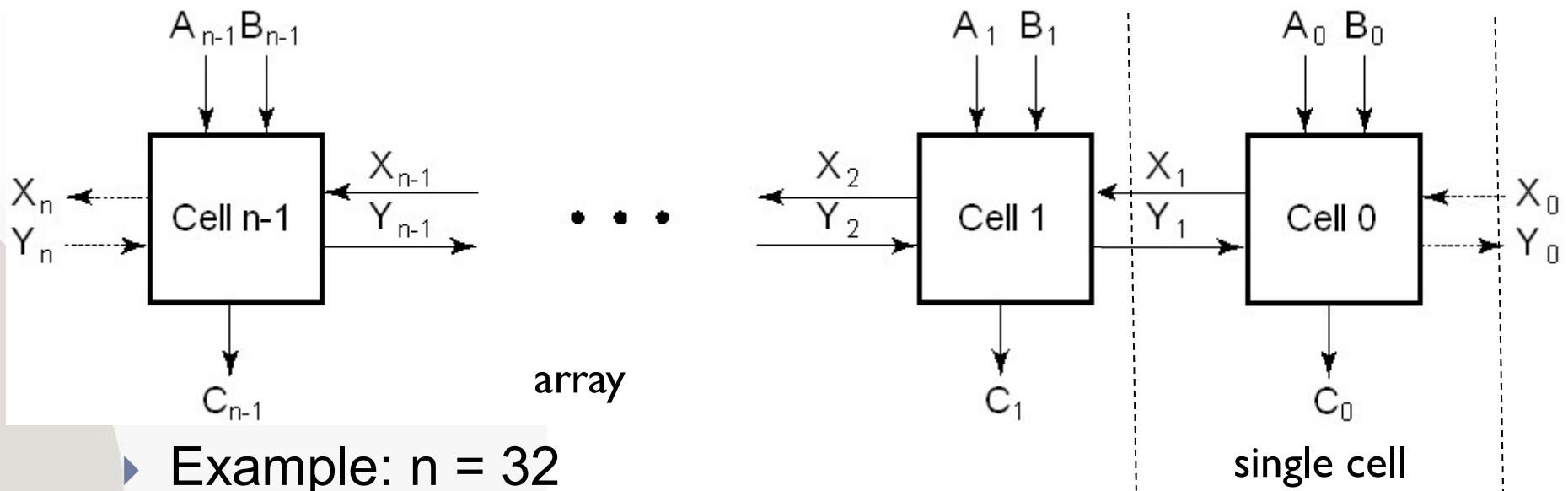

- ▶ Example: $n = 32$
 - ▶ Number of inputs = ?
 - ▶ Truth table rows = ?
 - ▶ Equations with up to ? input variables
 - ▶ Equations with huge number of terms
 - ▶ Design impractical!
- ▶ Iterative array takes advantage of the regularity to make design feasible: **Divide and Conquer!**

Arithmetic Functional Blocks: Addition

- ▶ Binary addition used frequently
- ▶ Addition Development:
 - ▶ *Half-Adder* (HA), a 2-input bit-wise addition functional block,
 - ▶ *Full-Adder* (FA), a 3-input bit-wise addition functional block,
 - ▶ *Ripple Carry Adder*, an iterative array to perform binary addition, and
 - ▶ *Carry-Look-Ahead Adder* (CLA), a hierarchical structure to improve performance.

Arithmetic Functional Block: Half-Adder

- ▶ A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+Y	+ 0	+ 1	+ 0	+ 1
C S	0 0	0 1	0 1	1 0

- ▶ A half adder adds two bits to produce a two-bit sum
- ▶ The sum is expressed as a sum bit , S and a carry bit, C
- ▶ The half adder can be specified as a truth table for S and C \Rightarrow

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Simplification: Half-Adder


- ▶ The K-Map for S, C is:
- ▶ This is a pretty trivial map!
By inspection:

$$S = X \cdot \bar{Y} + \bar{X} \cdot Y = X \oplus Y$$

- ▶ and

$$C = X \cdot Y$$

S		C	
	Y		Y
	0	0	1
X	1	X	1
	2	2	3

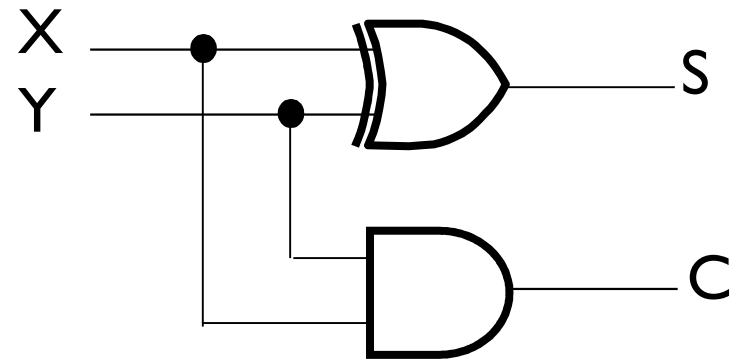

Arithmetic Functional Block: Full-Adder

- ▶ A full adder is similar to a half adder, but includes a carry-in bit from lower stages. Like the half-adder, it computes a sum bit, S and a carry bit, C.

- ▶ For a carry-in (Z) of 0, it is the same as the half-adder:

Z	0	0	0	0
X	0	0	1	1
+Y	+0	+1	+0	+1
C S	00	01	01	10

- ▶ For a carry-in (Z) of 1:

Z	1	1	1	1
X	0	0	1	1
+Y	+0	+1	+0	+1
C S	01	10	10	11

Logic Optimization: Full-Adder

Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full-Adder K-Map:

S		Y	
		0	1
X	0	1	1
	1	1	1
		Z	

C		Y	
		0	1
X	0	1	1
	1	1	1
		Z	

Equations: Full-Adder

- ▶ From the K-Map, we get:

$$\begin{aligned} S &= \overline{X}Y\overline{Z} + \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z + X\overline{Y}Z \\ C &= XY + XZ + YZ \end{aligned}$$

- ▶ The S function is the three-bit XOR function (Odd Function):

$$S = X \oplus Y \oplus Z$$

- ▶ The Carry bit C is 1 if both X and Y are 1 (the sum is 2), or if the sum is 1 and a carry-in (Z) occurs. Thus C can be re-written as:

$$C = XY + (X \oplus Y)Z$$


- ▶ The term $X \cdot Y$ is **carry generate**.
 - ▶ The term $X \oplus Y$ is **carry propagate**.
-

Implementation: Full Adder

- ▶ Full Adder Schematic
- ▶ Here X, Y, and Z, and C (from the previous pages) are A, B, C_i and C_o , respectively. Also,
 G = generate and
 P = propagate.
- ▶ Note: This is really a combination of a 3-bit odd function (for S) and Carry logic (for C_o):

(G = Generate) OR (P = Propagate AND C_i = Carry In)

$$C_o = G + P \cdot C_i$$

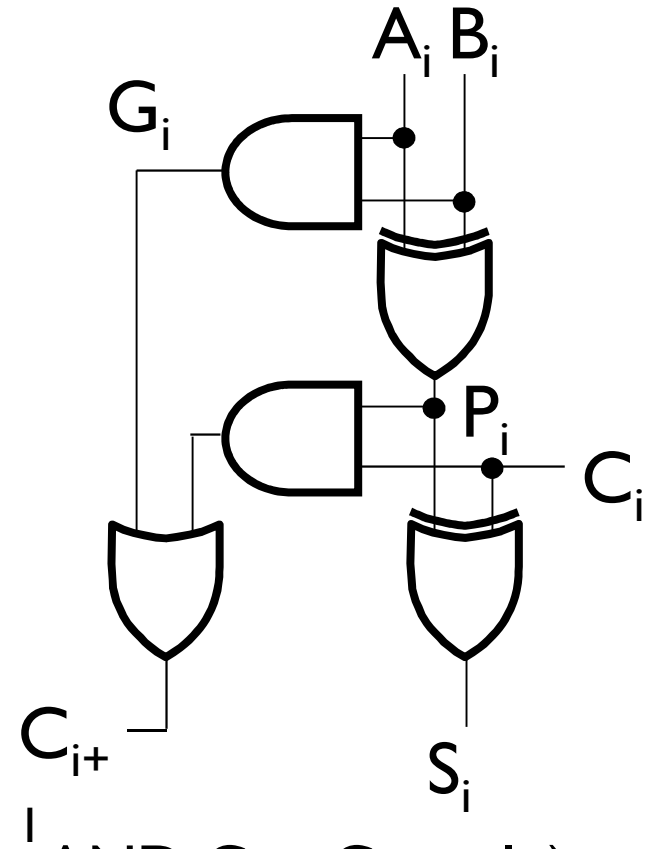


Binary Adders

- ▶ To add multiple operands, we “bundle” logical signals together into vectors and use functional blocks that operate on the vectors
- ▶ Example: 4-bit ripple carry adder: Adds input vectors $A(3:0)$ and $B(3:0)$ to get a sum vector $S(3:0)$
- ▶ Note: carry out of cell i becomes carry in of cell $i + 1$

Description	Subscript 3 2 1 0	Name
Carry In	0 1 1 0	C_i
Augend	1 0 1 1	A_i
Addend	0 0 1 1	B_i
Sum	1 1 1 0	S_i
Carry out	0 0 1 1	C_{i+1}

4-bit Ripple-Carry Binary Adder

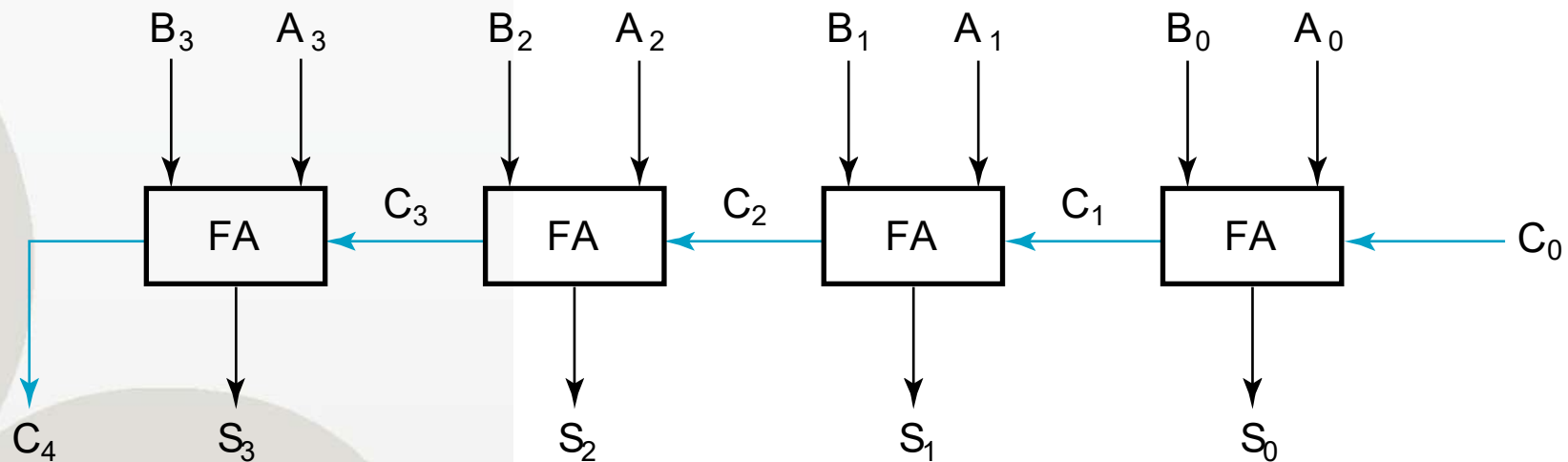
- ▶ A four-bit Ripple Carry Adder made from four 1-bit Full Adders:



Slow adder: many delays from input to output

Delay of a Full Adder

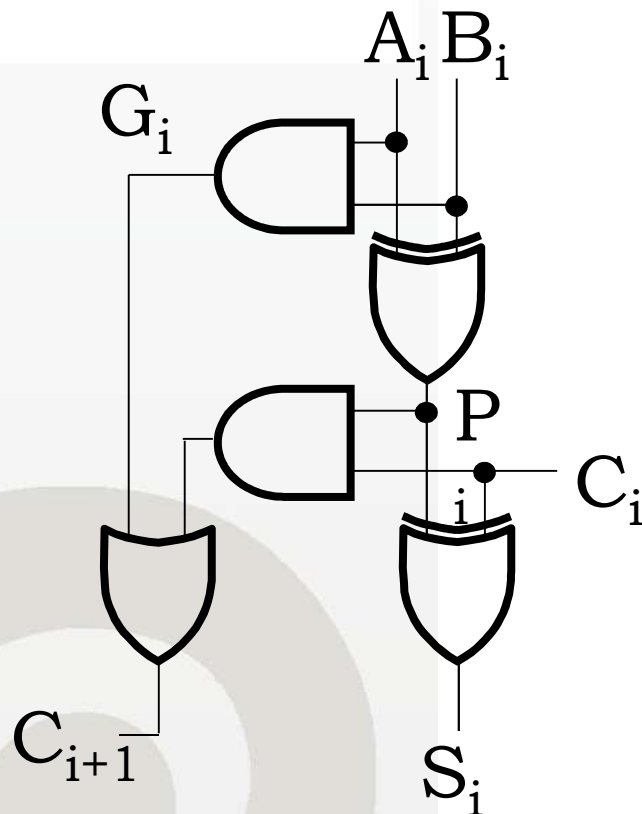- Assume that AND, OR gates have 1 **gate delay** and the XOR has 2 **gate delays**
- Delay of the Sum and Carry bit:



$$S_i = A_i \oplus B_i \oplus C_i$$

$$S_0 = A_0 \oplus B_0 \oplus C_0$$

2 delays

2+2=4 delays

$$C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i$$

$$C_1 = A_0 B_0 + (A_0 \oplus B_0) C_0$$


@2

@3

2+2=4 delays

Delay in a Ripple-carry adder

Example: 4-bit adder ($n=4$)

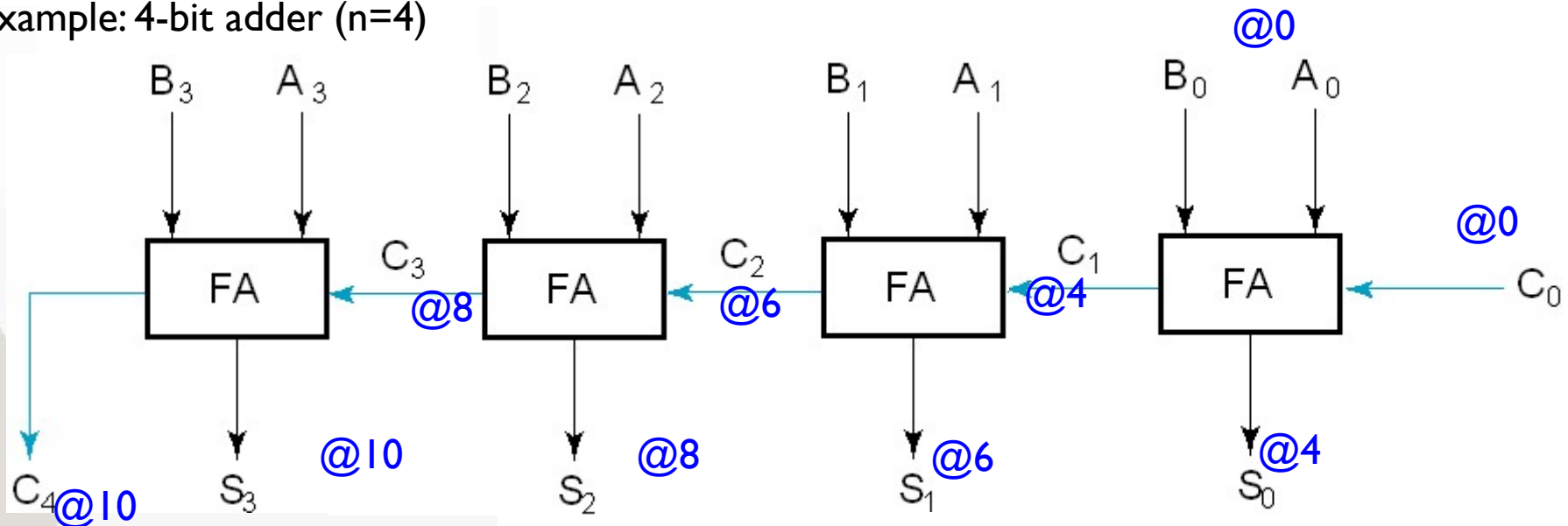

One problem with the addition of binary numbers is the length of time to propagate the ripple carry from the least significant bit to the most significant bit.

Example: 32-bit Ripple-carry has a unit gate delay of 1 ns.


- What is the total delay of the adder?
- What is the max frequency at which it can be clocked?

Carry Lookahead Adder

- ▶ Uses a different circuit to calculate the carry out (calculates it ahead), to speed up the overall addition
 - ▶ Requires more complex circuits.
 - ▶ Trade-off: speed vs. area (complexity, cost)
-

PFA generates G and P

4-bit Implementation

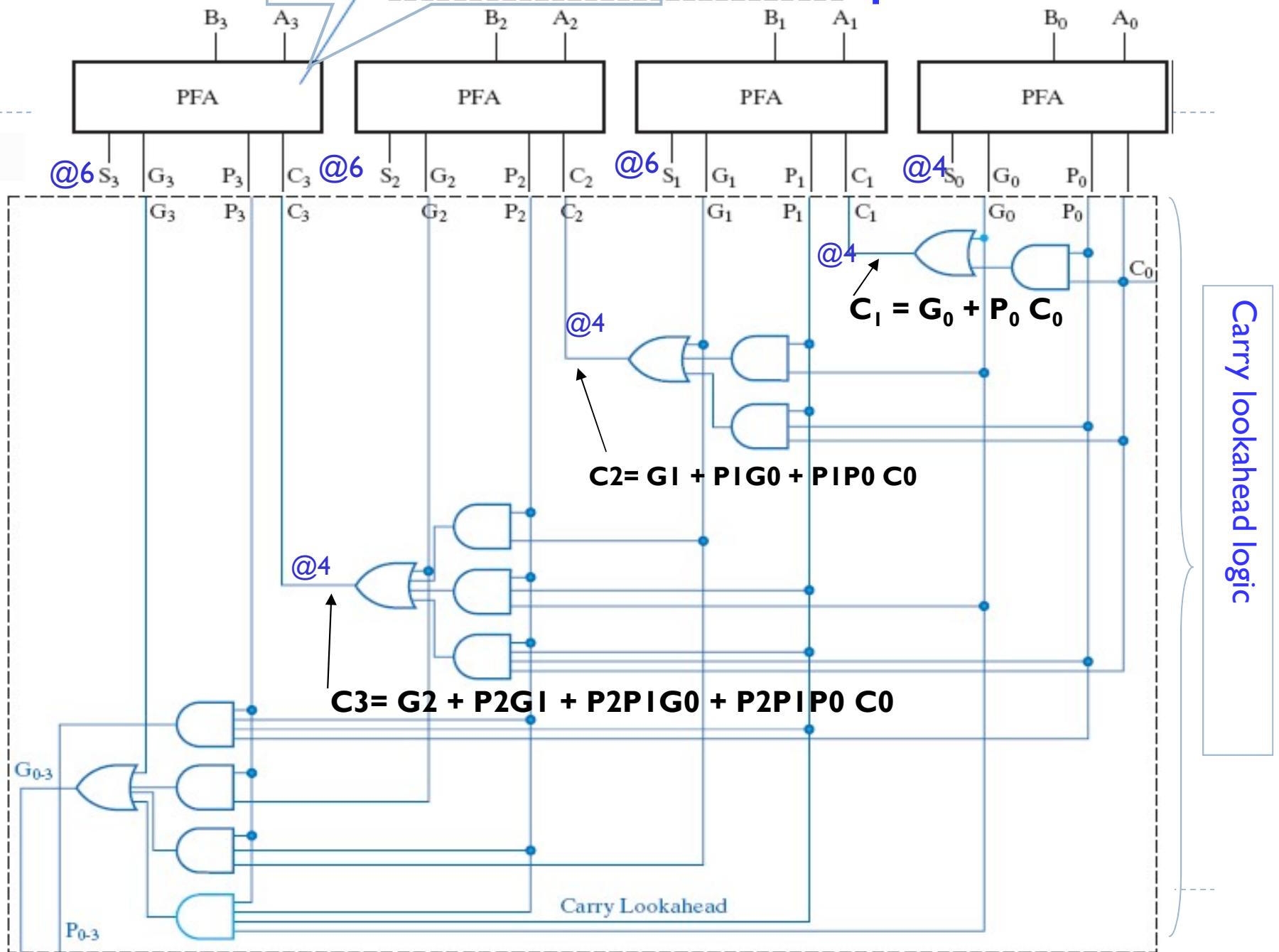

Unsigned Subtraction

- ▶ Algorithm:
 - ▶ Subtract N from M
 - ▶ If no end borrow occurs, then $M \geq N$, and the result is a non-negative number and correct.
 - ▶ If an end borrow occurs, then $N > M$ and the difference $M - N + 2^n$ is subtracted from 2^n , and a minus sign is appended to the result.


- ▶ Examples:

0	1
1001	0100
- 0111	- 0111
<u>0010</u>	<u>1101</u>

10000
- 1101
<u> </u>
(-) 0011

Unsigned Subtraction (continued)

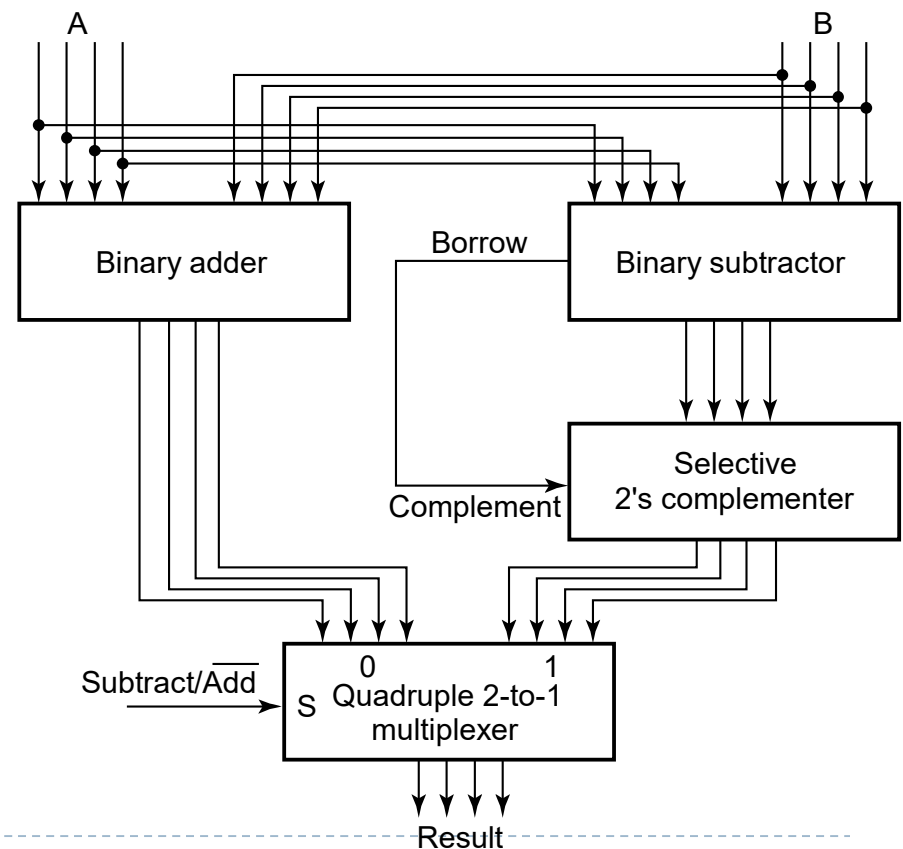- ▶ The subtraction, $2^n - N$, is taking the 2's complement of N
- ▶ To do both unsigned addition and unsigned subtraction requires:
 - ▶ Quite complex!
 - ▶ Goal: Shared simpler logic for both addition and subtraction
 - ▶ Introduce complements as an approach



Complements

- ▶ Two complements:
 - ▶ Diminished Radix Complement of N
 - ▶ $(r - 1)$'s complement for radix r
 - ▶ 1's complement for radix 2
 - ▶ Defined as $(r^n - 1) - N$
 - ▶ Radix Complement
 - ▶ r 's complement for radix r
 - ▶ 2's complement in binary
 - ▶ Defined as $r^n - N$
- ▶ Subtraction is done by adding the complement of the subtracted number
- ▶ If the result is negative, takes its 2's complement

Binary 1's Complement

- ▶ For $r = 2$, $N = 01110011_2$, $n = 8$ (8 digits):

$$(r^n - 1) = 256 - 1 = 255_{10} \text{ or } 11111111_2$$

- ▶ The 1's complement of 01110011_2 is then:

$$\begin{array}{r} 11111111 \\ - 01110011 \\ \hline 10001100 \end{array}$$

- ▶ Since the $2^n - 1$ factor consists of all 1's and since $1 - 0 = 1$ and $1 - 1 = 0$, the 1's complement is obtained by complementing each individual bit (bitwise NOT).

Binary 2's Complement

- ▶ For $r = 2$, $N = 01110011_2$, $n = 8$ (8 digits), we have:
 $(r^n) = 256_{10}$ or 100000000_2
- ▶ The 2's complement of 01110011 is then:

$$\begin{array}{r} 100000000 \\ - 01110011 \\ \hline 10001101 \end{array}$$

- ▶ Note the result is the 1's complement plus 1, a fact that can be used in designing hardware

Alternate 2's Complement Method

- ▶ Given: an n -bit binary number, beginning at the least significant bit and proceeding upward:
 - ▶ Copy all least significant 0's
 - ▶ Copy the first 1
 - ▶ Complement all bits thereafter.

- ▶ 2's Complement Example:

10010100

- ▶ Copy underlined bits:

100

- ▶ and complement bits to the left:

01101100

Subtraction with 2's Complement

- ▶ For n-digit, unsigned numbers M and N, find $M - N$ in base 2:
 - ❑ Add the 2's complement of N to M:
$$M + (2^n - N) = M - N + 2^n$$
 - ❑ If $M \geq N$, the sum produces end carry 2^n which is discarded; from above, $M - N$ remains.
 - ❑ If $M < N$, the sum does not produce an end carry, since it is equal to $2^n - (N - M)$, the 2's complement of $(N - M)$.
 - ❑ To obtain the result $-(N - M)$, take the 2's complement of the sum and place a $-$ to its left.

2's Complement Subtraction Example 1

- Find $01010100_2 - 01000011_2$

$$\begin{array}{r} 01010100 \\ - 01000011 \\ \hline \end{array} \xrightarrow{\text{2's comp}} \begin{array}{r} 1 \quad 01010100 \\ + \quad 10111101 \\ \hline 00010001 \end{array}$$

- The carry of 1 indicates that no correction of the result is required.

2's Complement Subtraction Example 2

- Find $01000011_2 - 01010100_2$

$$\begin{array}{r} 01000011 \\ - 01010100 \\ \hline \end{array} \xrightarrow{\text{2's comp}} \begin{array}{r} 0 \quad 01000011 \\ + 10101100 \\ \hline 11101111 \\ \hline 00010001 \end{array}$$

- The carry of 0 indicates that a correction of the result is required.
- Result = $-(00010001)$

2's Complement Adder/Subtractor


- Subtraction can be done by addition of the 2's Complement.

1. Complement each bit (1's Complement.)
2. Add 1 to the result.

- The circuit shown computes $A + B$ and $A - B$:

- For $S = 1$, subtract, the 2's complement of B is formed by using XORs to form the 1's comp and adding the 1 applied to C_0 .

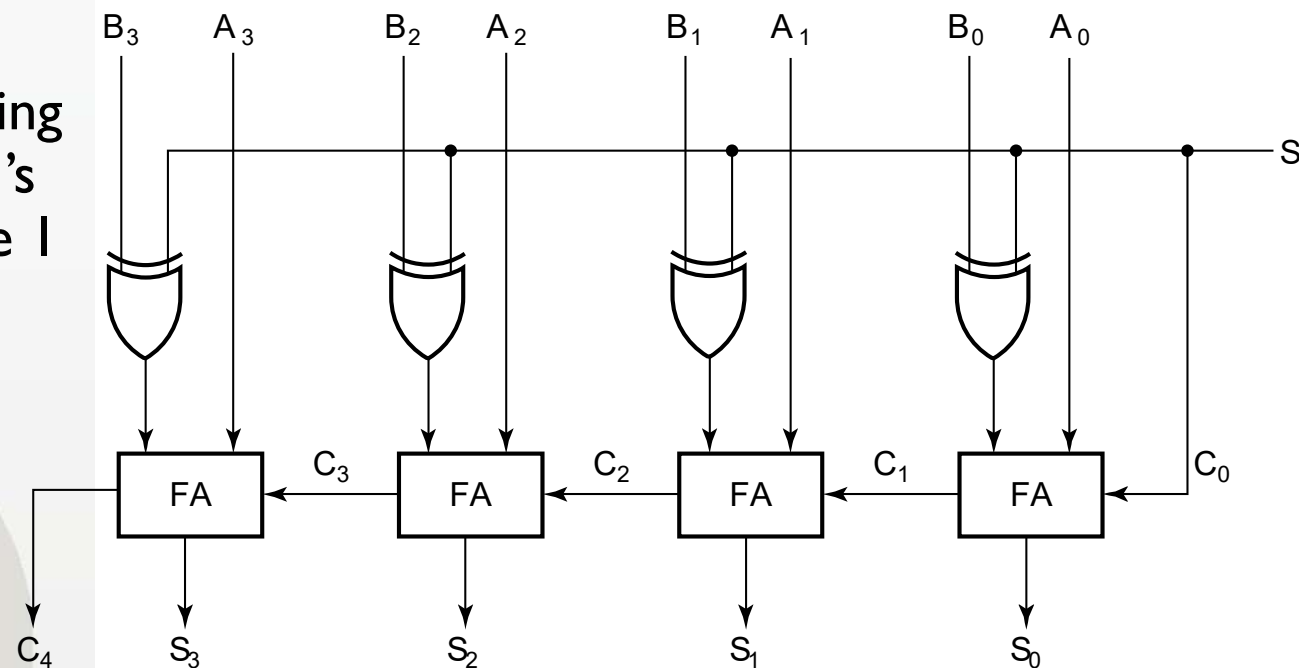- For $S = 0$, add, B is passed through unchanged



Signed Integers

- ▶ Positive numbers and zero can be represented by unsigned n -digit, radix r numbers. We need a representation for negative numbers.
- ▶ To represent a sign (+ or –) we need exactly one more bit of information (1 binary digit gives $2^1 = 2$ elements which is exactly what is needed).
- ▶ Since computers use binary numbers, by convention, the most significant bit is interpreted as a sign bit:

$$s \ a_{n-2} \ \dots \ a_2 a_1 a_0$$

where:

$s = 0$ for Positive numbers

$s = 1$ for Negative numbers

and $a_i = 0$ or 1 represent the magnitude in some form.

Exercise

- ▶ Give the sign+magnitude, 1's complement and 2's complement of (using minimal required bits):

	<u>Sign+Mag</u>	<u>One's compl.</u>	<u>Two's compl.</u>
+2	010	010	010
- 2	110	101	110
+3	011	011	011
- 3	111	100	101
+0	000	000	000
- 0	100	111	000

Signed 2's complement system

- ▶ Positive numbers are unchanged
- ▶ Negative numbers: take 2's complement
- ▶ Example for 4-bit word:

0	0000
+1	0001
+2	0010
+3	0011
+4	0100
+5	0101
+6	0110
+7	0111

-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

- 0 indicates positive and 1 negative numbers
- 7 positive numbers and 8 negative ones

2's Complement Arithmetic

▶ Addition: Simple rule

- ▶ Represent negative number by its 2's complement. Then, add the numbers including the sign bits, discarding a carry out of the sign bits (2's complement):
- ▶ Indeed, e.x. $M + (-N) \rightarrow M + (2^n - N)$
- ▶ If $M \geq N$: $(M - N) + 2^n$ ignore carry out: $M - N$ is the answer in two's complement
- ▶ If $M \leq N$: $(M - N) + 2^n = 2^n - (N - M)$ which is 2's complement of the (negative) number $(M - N)$: $-(N - M)$.

▶ Subtraction: $M - N \rightarrow M + (2^n - N)$

Form the complement of the number you are subtracting and follow the rules for addition.

Signed 2's Complement Examples

▶ Example 1:
$$\begin{array}{r} 1101 \\ + \underline{0011} \end{array}$$

▶ Example 2:
$$\begin{array}{r} 1101 \\ - \underline{0011} \end{array}$$

▶ Example 3: $(5 - 11)_{10}$ (using 2's compl.)

Any Questions?

