

# **ROBT206 – Microcontrollers with Lab**

## **Lecture 20 – Register Cells, Buses**

**5 April, 2018**

# Course Logistics

---

## Important Dates and Tasks

Homework #4 due to end of 14 April

7.3, 7.4, 7.5, 7.10, 7.11, 7.12, 7.15, 7.19, 7.21, 7.22, 7.28, 7.37

# Topics



---

## Today's Topics

- Register cell design
- Multiplexer and bus-based transfers for multiple registers
- Serial transfers and micro-operations
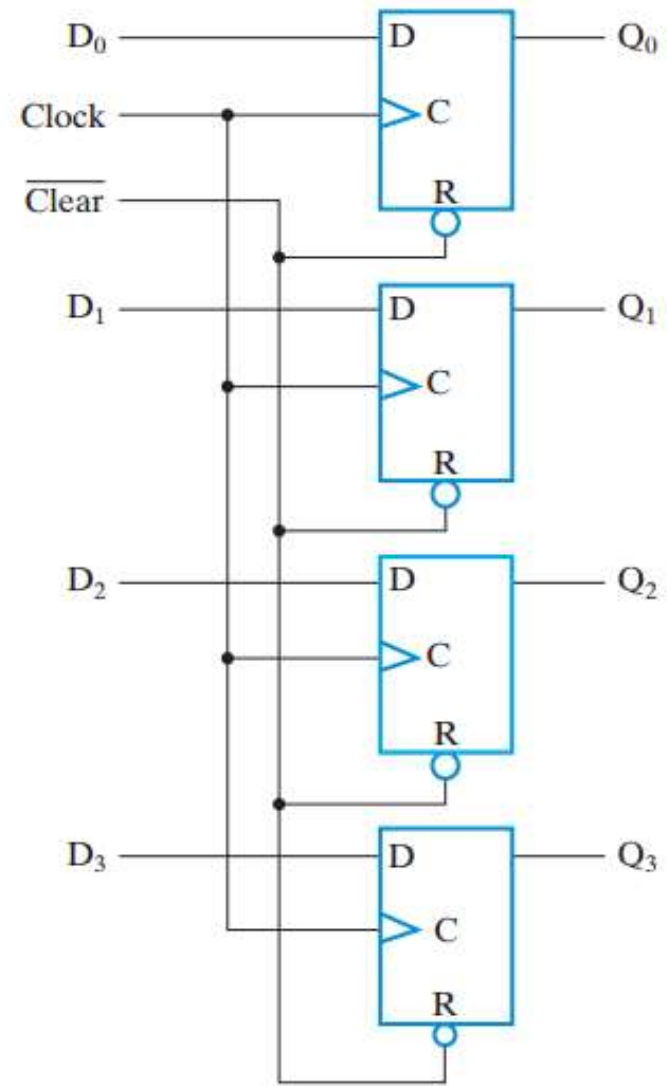 
# Recap: Register with Parallel Load

- ▶ Register: Group of Flip-Flops
- ▶ Ex: D Flip-Flops
- ▶ Holds a Word (Nibble) of Data
- ▶ Loads in Parallel on Clock Transition
- ▶ Asynchronous Clear (Reset)



# Register Cell Design

---

- ▶ Assume that a register consists of identical cells
- ▶ Then register design can be approached as follows:
  - ▶ Design representative cell for the register
  - ▶ Connect copies of the cell together to form the register
  - ▶ Applying appropriate “boundary conditions” to cells that need to be different
- ▶ Register cell design is the first step of the above process

# Register Cell Specifications

---

- ▶ A register
- ▶ Data inputs to the register
- ▶ Control input combinations to the register
  - ▶ **Example 1: Not encoded**
    - ▶ Control inputs: **Load, Shift, Add**
    - ▶ At most, one of **Load, Shift, Add** is 1 for any clock cycle  
(0,0,0), (1,0,0), (0,1,0), (0,0,1)
  - ▶ **Example 2: Encoded**
    - ▶ Control inputs: S1, S0
    - ▶ All possible binary combinations on S1, S0  
(0,0), (0,1), (1,0), (1,1)

# Register Cell Specifications

---

- ▶ A set of register functions (typically specified as register transfers)

- ▶ **Example:**

- Load:  $A \leftarrow B$

- Shift:  $A \leftarrow \text{sr}B$

- Add:  $A \leftarrow A + B$

- ▶ A hold state specification


- ▶ **Example:**

- ▶ Control inputs: Load, Shift, Add

- ▶ If all control inputs are 0, hold the current register state
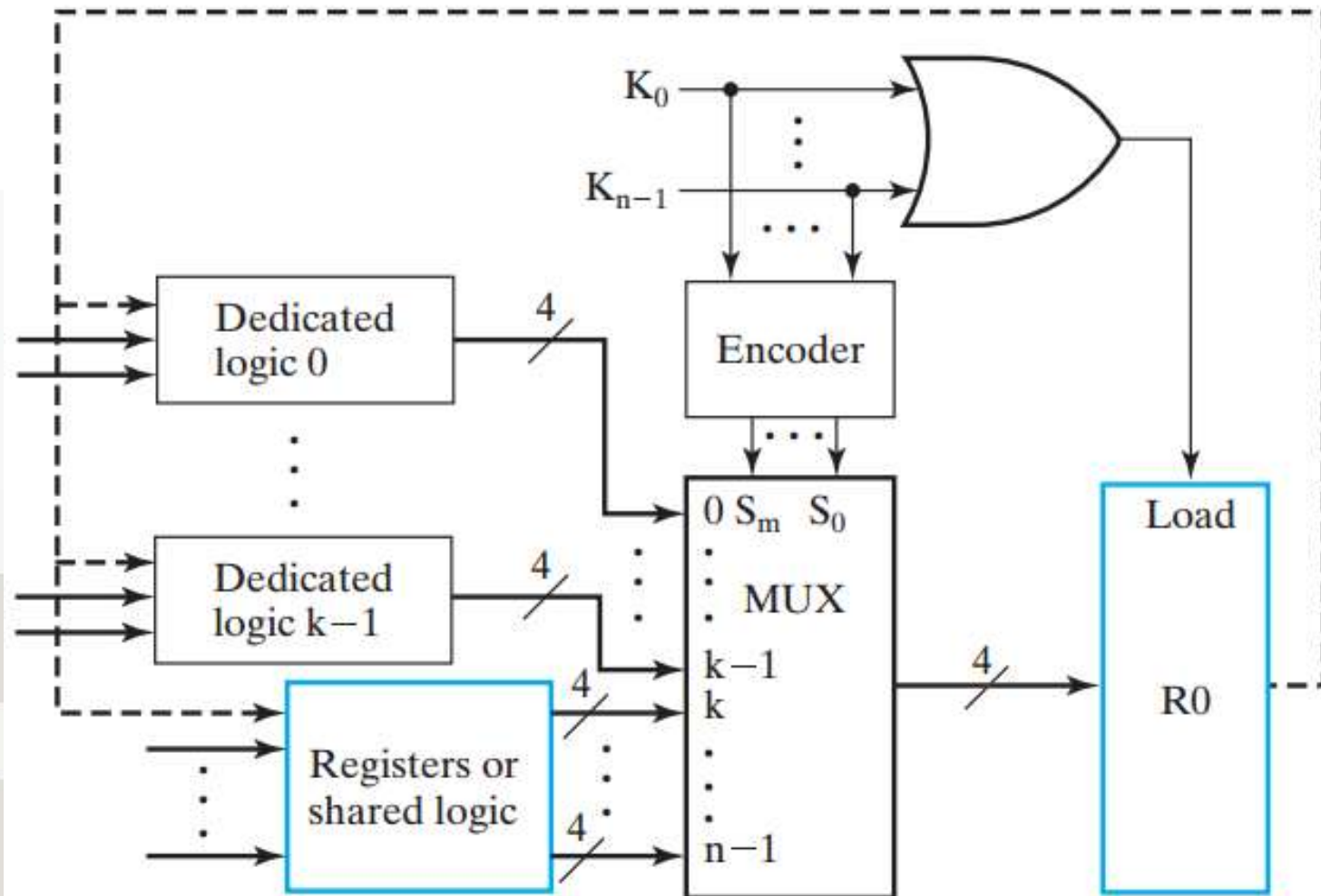
# Recap: Multiplexer Approach

- Uses an n-input multiplexer with a variety of transfer sources and functions





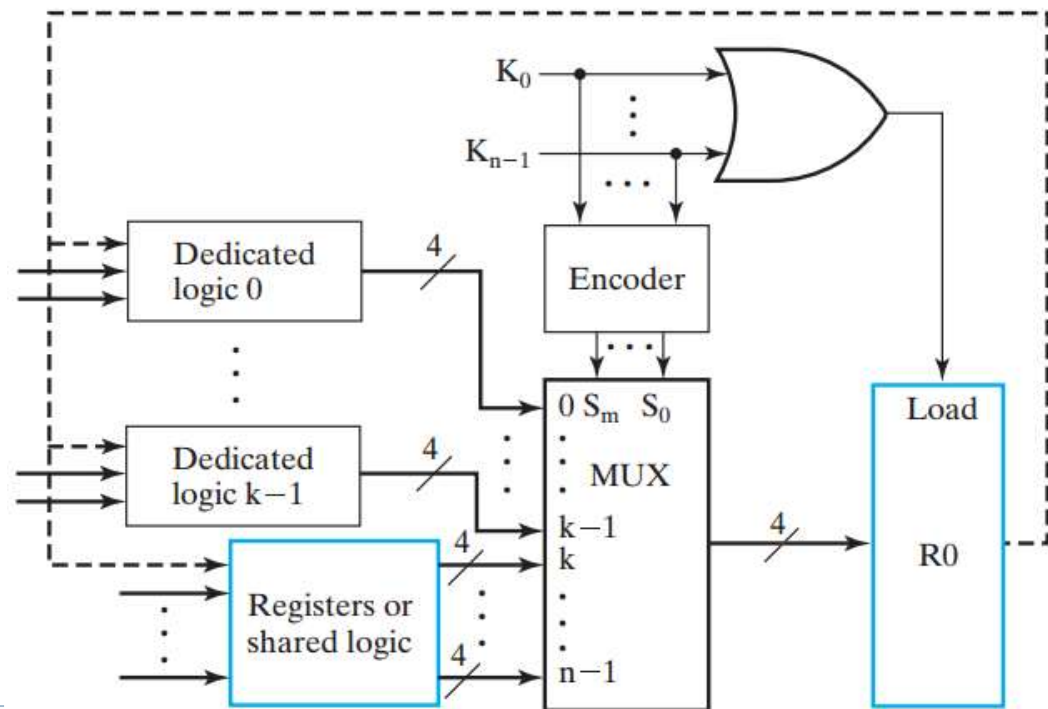
# Recap: Multiplexer Approach

- ▶ Load enable by OR of control signals  $K_0, K_1, \dots, K_{n-1}$ 
  - assumes no load for 00...0
- ▶ Use:
  - ▶ **Encoder + Multiplexer (shown) or**
  - ▶  **$n \times 2$  AND-OR**

to select sources and/or transfer functions



# Example 1: Register Cell Design

---

- ▶ Register A (m-bits) Specification:
  - ▶ Data input: B
  - ▶ Control inputs (AND, OR, EXOR)
  - ▶ Control input combinations (0,0,0), (0,0,1) (0,1,0)(1,0,0)
  - ▶ Register transfers:
    - ▶ AND:  $A \leftarrow A \wedge B$
    - ▶ OR:  $A \leftarrow A \vee B$
    - ▶ EXOR:  $A \leftarrow B \oplus A$
    - ▶ Hold state: (0,0,0)
- ▶ Load Control  
Load = AND+OR + EXOR

# Sequential Circuit Design Approach

---

- ▶ Find a state diagram or state table
  - ▶ Note that there are only two states with the state assignment equal to the register cell output value
- ▶ For optimization:
  - ▶ Use K-maps for up to 4 to 6 variables
  - ▶ Otherwise, use computer-aided or manual optimization

# Example 1 Again

## State Table:

Present State A	Next State A(t + 1)						
	(AND = 0) ·(EXOR=0) ·(OR=0)	(OR = 1) ·(B=0)	(OR = 1) ·(B=1)	(EXOR = 1) ·(B=0)	(EXOR = 1) ·(B=1)	(AND = 1) ·(B=0)	(AND = 1) ·(B=1)
0	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1

- ▶ A is a state variable and output,
- ▶ AND, EXOR, OR and B are inputs
- ▶ Don't care conditions (for AND = OR = EXOR = 1)

# Example 1 Continued

---

- ▶ The resulting SOP equation:

$$D_i = A(t + 1) = \text{AND } A_i B_i + \text{EXOR } (A_i \bar{B}_i + \bar{A}_i B_i) + \text{OR } (A_i + B_i) + \overline{\text{AND}} \overline{\text{EXOR}} \overline{\text{OR}} A_i$$

- ▶ Note that control variables AND, OR, EXOR can be shared between register cells since they are the same for each cell
- ▶ Factor including variables A and B are implemented in each cell



# Example 1 Continued

- ▶ Separating factor involving condition variables only, the governing equation is rewritten as

$$\begin{aligned} D_i &= (\text{AND} + \text{OR} + \overline{\text{AND}} \overline{\text{EXOR}} \overline{\text{OR}}) (A_i B_i) \\ &+ (\text{EXOR} + \text{OR} + \overline{\text{AND}} \overline{\text{EXOR}} \overline{\text{OR}}) (A_i \bar{B}_i) + (\text{EXOR} + \text{OR}) (\bar{A}_i B_i) \\ &= (\text{AND} + \text{OR} + \overline{\text{EXOR}}) (A_i B_i) + (\text{EXOR} + \text{OR} + \overline{\text{AND}}) (A_i \bar{B}_i) \\ &\quad + (\text{EXOR} + \text{OR}) (\bar{A}_i B_i) \end{aligned}$$

- ▶  $C_1 = \text{OR} + \text{AND} + \overline{\text{EXOR}}$
- ▶  $C_2 = \text{OR} + \text{EXOR}$
- ▶  $C_3 = C_2 + \overline{\text{AND}}$
- ▶  $D_i = C_1 A_i B_i + C_3 A_i \bar{B}_i + C_2 \bar{A}_i B_i$

# Example 1 Continued

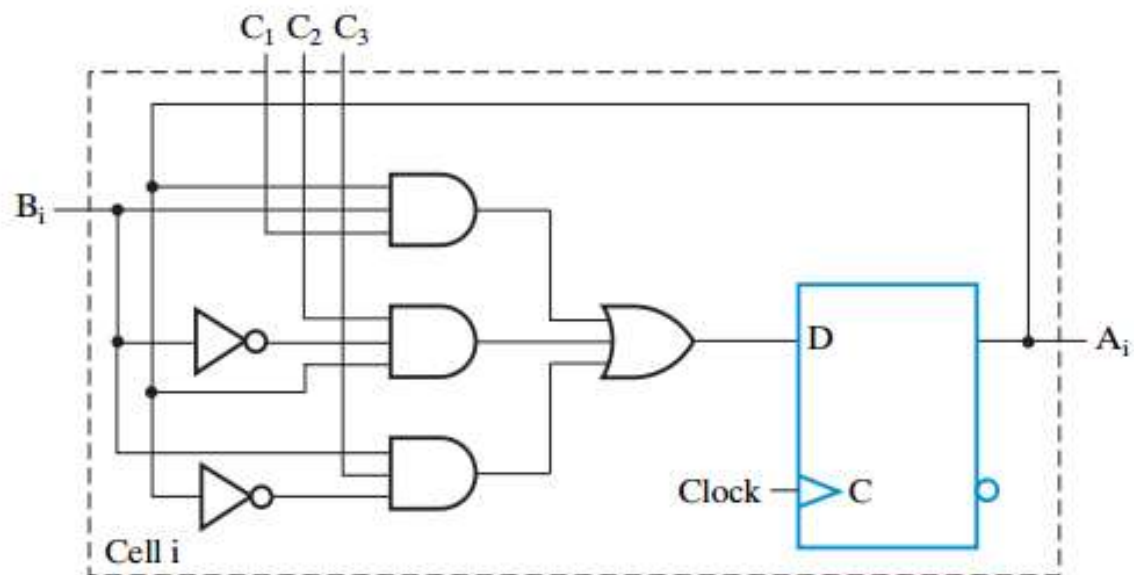 

# Multiplexer and Bus-Based Transfers for Multiple Registers


---

- ▶ Multiplexer dedicated to each register
- ▶ Shared transfer paths for registers
  - ▶ A shared transfer object is called a *bus* (Plural: *buses*)
- ▶ Bus implementation using:
  - ▶ multiplexers
  - ▶ three-state nodes and drivers
- ▶ In most cases, the number of bits is the length of the receiving register


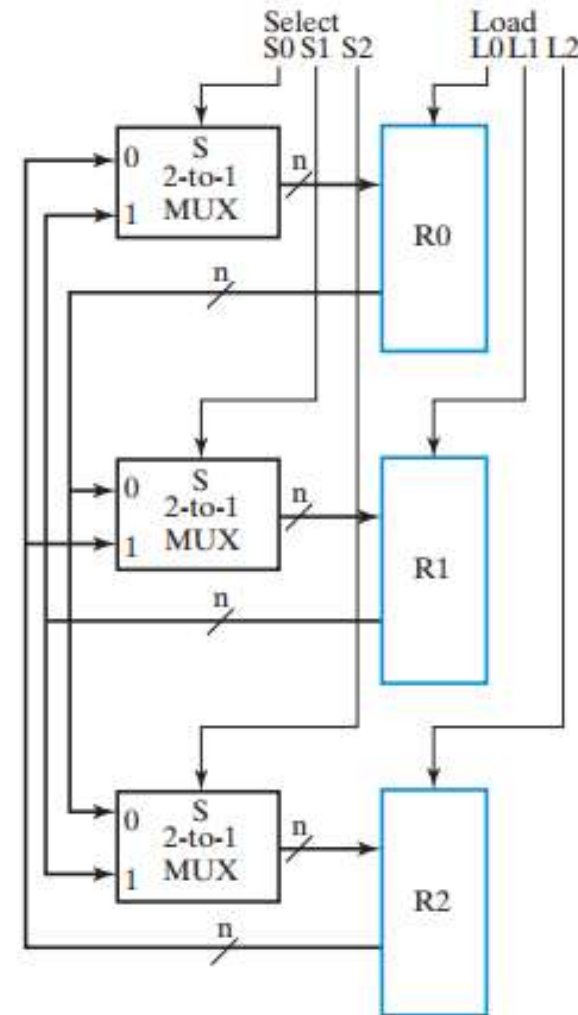
# Dedicated MUX-Based Transfers

- ▶ Multiplexer connected to each register input produces a very flexible transfer structure =>
- ▶ Characterize the simultaneous transfers possible with this structure.




(a) Dedicated multiplexers

# Multiplexer Bus

- ▶ A single bus driven by a multiplexer lowers cost, but limits the available transfers =>
- ▶ Characterize the simultaneous transfers possible with this structure.


Register Transfer	Select		Load		
	S1	S0	L2	L1	L0
$R0 \leftarrow R2$	1	0	0	0	1
$R0 \leftarrow R1, R2 \leftarrow R1$	0	1	1	0	1
$R0 \leftarrow R1, R1 \leftarrow R0$	Impossible				

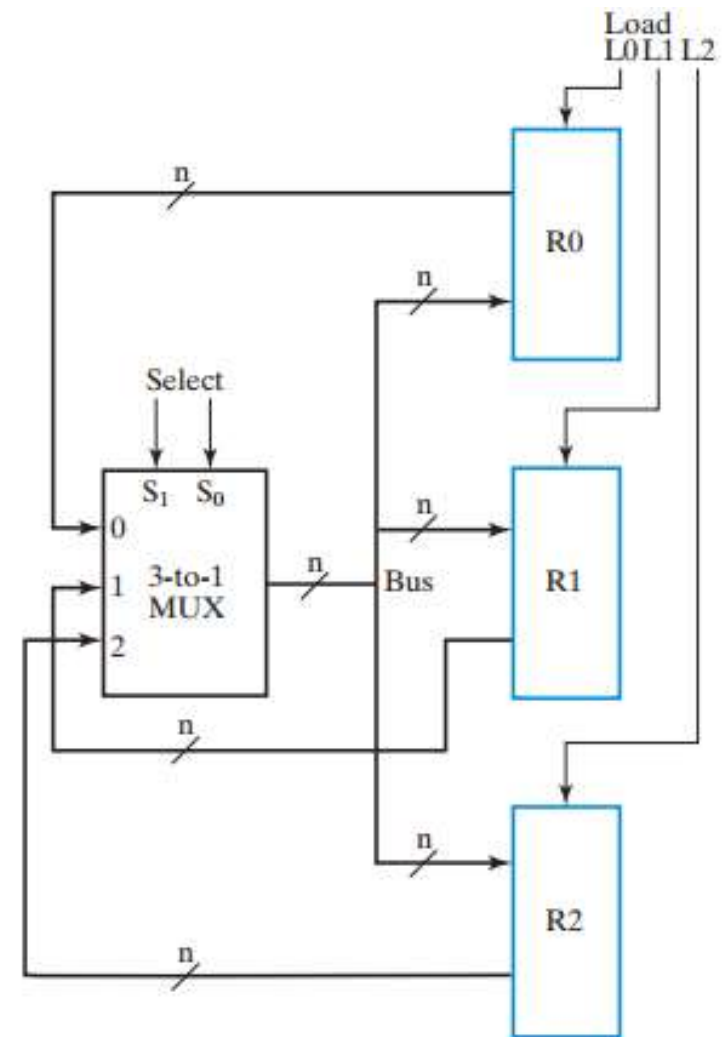

 
(b) Single bus

- ▶ Cost is further reduced if transfers are limited
- ▶ Characterize the simultaneous transfers possible with this structure.

- ▶ The 3-input MUX can be replaced by a 3-state node (bus) and 3-state buffers.
- ▶ Cost is further reduced, but transfers are limited
- ▶ Characterize the simultaneous transfers possible with this structure.



 (a) Register with bidirectional input-output lines and symbol



(c) Three-state bus using registers with bidirectional lines

# Serial Transfers and Micro-operations

---

- ▶ Serial Transfers
  - ▶ Used for “narrow” transfer paths
  - ▶ Example 1: Telephone or cable line
    - ▶ Parallel-to-Serial conversion at source
    - ▶ Serial-to-Parallel conversion at destination
- ▶ Serial micro-operations
  - ▶ Example: Addition


# Serial Micro-operations

---

- ▶ By using two shift registers for operands, a full adder, and a flip flop (for the carry), we can add two numbers serially, starting at the least significant bit.
- ▶ Serial addition is a low cost way to add large numbers of operands, since a “tree” of full adder cells can be made to any depth, and each new level doubles the number of operands.
- ▶ Other operations can be performed serially as well, such as parity generation/checking or more complex error-check codes.
- ▶ Shifting a binary number left is equivalent to multiplying by 2.
- ▶ Shifting a binary number right is equivalent to dividing by 2.
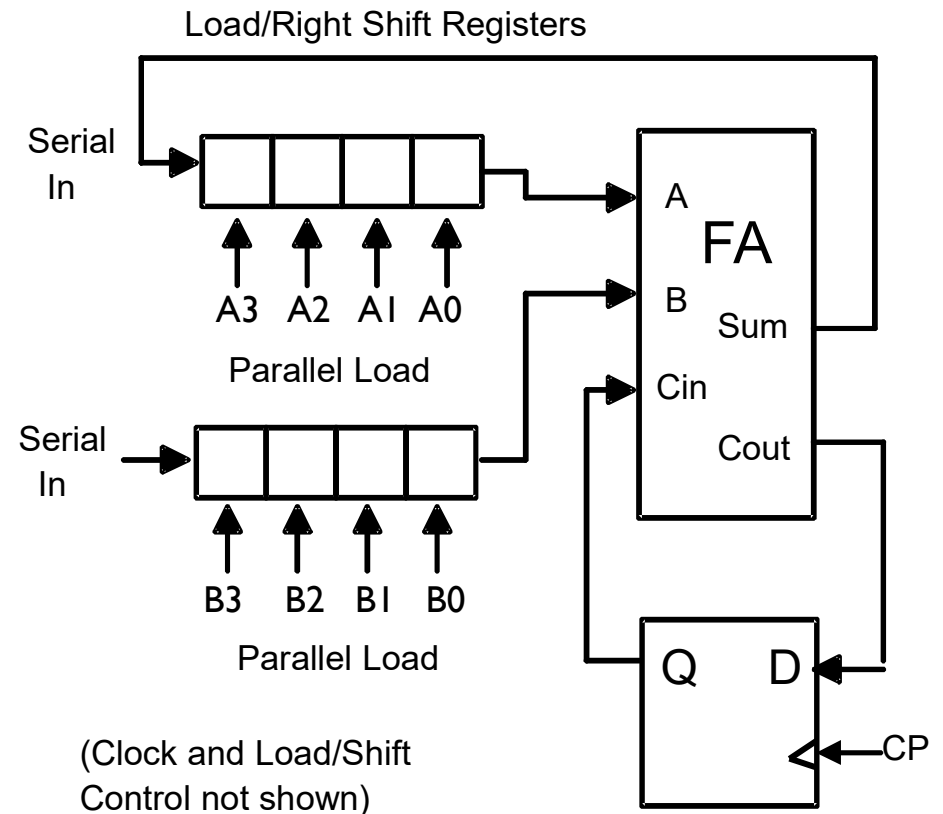
# Serial Adder

- ▶ The circuit shown uses two shift registers for operands A(3:0) and B(3:0).
- ▶ A full adder, and one more flip flop (for the carry) is used to compute the sum.
- ▶ The result is stored in the A register and the final carry in the flip-flop
- ▶ With the operands and the result in shift registers, a tree of full adders can be used to add a large number of operands. Used as a common digital signal processing technique.



# Any Questions?

---

