

ROBT206 – Microcontrollers with Lab

Lecture 19 – Counters

3 April, 2018

Topics

Today's Topics



- Microoperations on single register (continued)
 - Counters

Counters

- ▶ **Counters** are sequential circuits which "count" through a specific state sequence. They can **count up**, **count down**, or **count through other fixed sequences**. Two distinct types are in common usage:
 - ▶ **Ripple Counters**
 - ▶ Clock connected to the flip-flop clock input on the LSB bit flip-flop
 - ▶ For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous!
 - ▶ Output change is delayed more for each bit toward the MSB.
 - ▶ Resurgent because of low power consumption
 - ▶ **Synchronous Counters**
 - ▶ Clock is directly connected to the flip-flop clock inputs
 - ▶ Logic is used to implement the desired state sequencing


Ripple Counter

  - ▶ How does it work?
 - ▶ When there is a positive edge on the clock input of A, A complements
 - ▶ The clock input for flip-flop B is the complemented output of flip-flop A
 - ▶ When flip-flop A changes from 1 to 0, there is a positive edge on the clock input of B causing B to complement



Ripple Counter

 - ▶ The arrows show the cause-effect relationship from the prior slide
- ▶ The corresponding sequence of states $(B,A) = (0,0),(0,1),(1,0),(1,1),(0,0),(0,1), \dots$
- ▶ Each additional bit, C, D, ... behaves like bit B, changing half as frequently as the bit before it.
- ▶ For 3 bits: $(C,B,A) = (0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0), (1,1,1), (0,0,0), \dots$




Ripple Counter (Continued)

- ▶ These circuits are called *ripple counters* because each edge sensitive transition (positive in the example) causes a change in the next flip-flop's state.
- ▶ The changes “ripple” upward through the chain of flip-flops, i. e., each transition occurs after a clock-to-output delay from the stage before.


Ripple Counter (Continued)

 - ▶ Starting with $C = B = A = 1$, equivalent to $(C,B,A) = 7$ base 10, the next clock increments the count to $(C,B,A) = 0$ base 10. In fine timing detail:
 - ▶ The clock to output delay t_{PHL} causes an increasing delay from clock edge for each stage transition.
 - ▶ Thus, the count “ripples” from least to most significant bit.
 - ▶ For n bits, total worst case delay is $n t_{PHL}$.




Synchronous Counters

 - ▶ To eliminate the "ripple" effects, use a common clock for each flip-flop and a combinational circuit to generate the next state.
- ▶ For an up-counter, use an incrementer =>



Synchronous Counters

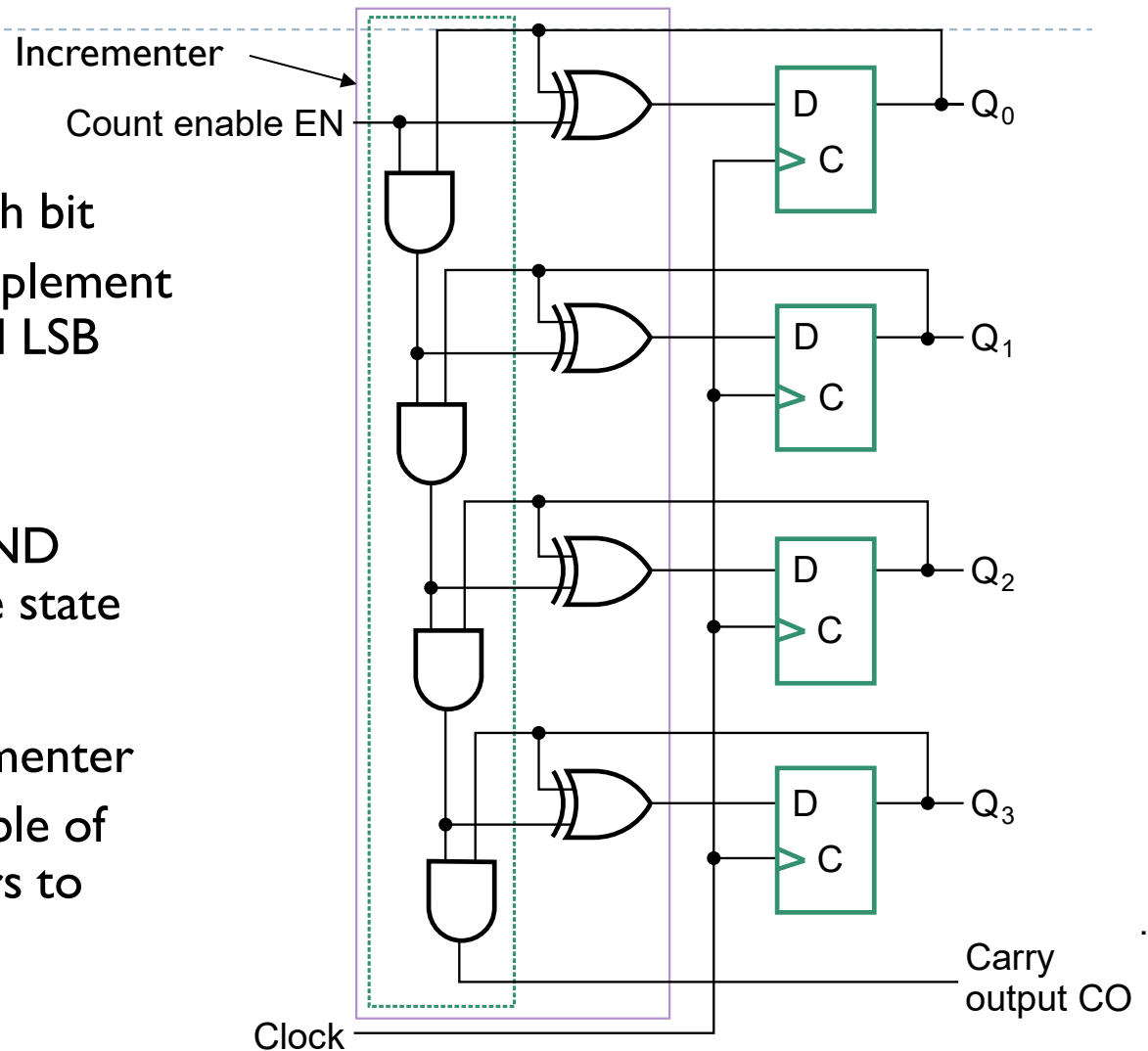- ▶ Internal details →
- ▶ Internal Logic
 - ▶ XOR complements each bit
 - ▶ AND chain causes complement of a bit if all bits toward LSB from it equal 1
- ▶ Count Enable
 - ▶ Forces all outputs of AND chain to 0 to “hold” the state
- ▶ Carry Out
 - ▶ Added as part of incrementer
 - ▶ Connect to Count Enable of additional 4-bit counters to form larger counters




(a) Logic Diagram-Serial Gating


Synchronous Counters

- ▶ Carry chain
 - ▶ series of AND gates through which the carry “ripples”
 - ▶ Yields long path delays
 - ▶ Called *serial gating*
- ▶ Replace AND carry chain with ANDs => in parallel
 - ▶ Reduces path delays
 - ▶ Called *parallel gating*
 - ▶ Like carry lookahead
 - ▶ Lookahead can be used on COs and ENs to prevent long paths in large counters

- ▶ Symbol for Synchronous Counter

 

Symbol

 


Logic Diagram-Parallel Gating

Counter with Parallel Load

- ▶ Add path for input data
 - ▶ enabled for Load = 1
- ▶ Add logic to:
 - ▶ disable count logic for Load = 1
 - ▶ disable feedback from outputs for Load = 1
 - ▶ enable count logic for Load = 0 and Count = 1
- ▶ The resulting function table:

| Load | Count | Action |
|------|-------|-----------------------|
| 0 | 0 | Hold Stored Value |
| 0 | 1 | Count Up Stored Value |
| 1 | X | Load D |

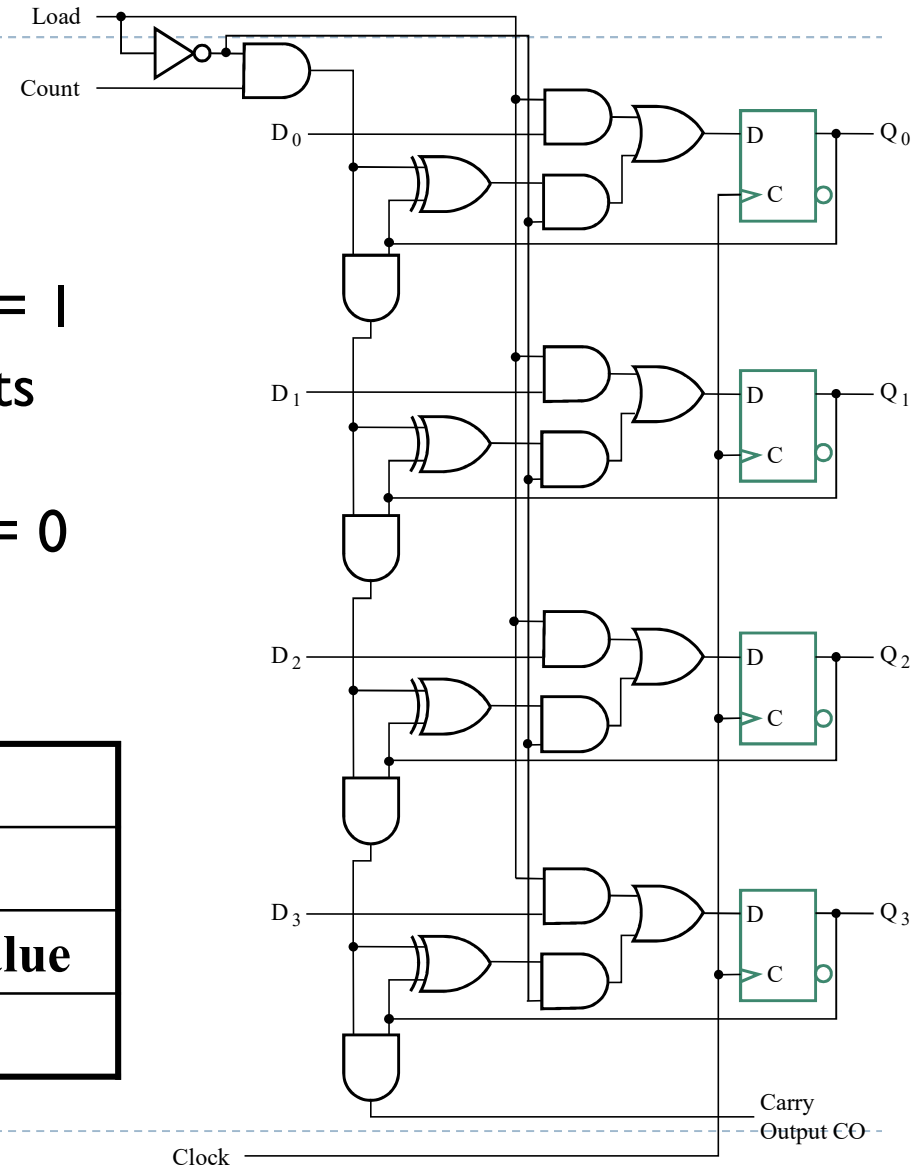

Design Example: Synchronous BCD Counter

- ▶ Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- ▶ State Table =>
- ▶ Input combinations 1010 through 1111 are don't cares

| Current State | | | | | Next State | | | |
|---------------|----|----|----|--|------------|----|----|----|
| Q8 | Q4 | Q2 | Q1 | | Q8 | Q4 | Q2 | Q1 |
| 0 | 0 | 0 | 0 | | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | | 0 | 0 | 0 | 0 |

Synchronous BCD (Continued)

- ▶ Use K-Maps to two-level optimize the next state equations and manipulate into forms containing XOR gates:

$$D1 = \overline{Q1}$$

$$D2 = Q2 \oplus Q1 \overline{Q8}$$

$$D4 = Q4 \oplus Q1 Q2$$


$$D8 = Q8 \oplus (Q1 Q8 + Q1 Q2 Q4)$$

- ▶ The logic diagram can be drawn from these equations
 - ▶ An asynchronous or synchronous reset should be added
- ▶ For the BCD counter design, if an invalid state is entered, return to a valid state occurs within two clock cycles

Synchronous BCD (Continued)

- Find the actual values of the six next states for the don't care combinations from the equations
- Find the overall state diagram to assess behavior for the don't care states (states in decimal)

| Present State | | | | Next State | | | |
|---------------|----|----|----|------------|----|----|----|
| Q8 | Q4 | Q2 | Q1 | Q8 | Q4 | Q2 | Q1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |

 

Synchronous BCD


- ▶ For the BCD counter design, if an invalid state is entered, return to a valid state occurs within two clock cycles
- ▶ Is this adequate? If not:
 - ▶ Is a signal needed that indicates that an invalid state has been entered? What is the equation for such a signal?
 - ▶ Does the design need to be modified to return from an invalid state to a valid state in one clock cycle?
 - ▶ Does the design need to be modified to return from a invalid state to a specific state (such as 0)?
- ▶ The action to be taken depends on:
 - ▶ the application of the circuit
 - ▶ design group policy

Counting Modulo N

- ▶ The following techniques use an n -bit binary counter with asynchronous or synchronous clear and/or parallel load:
 - ▶ Detect a *terminal count* of N in a Modulo- N count sequence to asynchronously Clear the count to 0 or asynchronously Load in value 0 (These lead to counts which are present for only a very short time and can fail to work for some timing conditions!)
 - ▶ Detect a terminal count of $N - 1$ in a Modulo- N count sequence to Clear the count synchronously to 0
 - ▶ Detect a terminal count of $N - 1$ in a Modulo- N count sequence to synchronously Load in value 0
 - ▶ Detect a terminal count and use Load to preset a count of the terminal count value minus $(N - 1)$
- ▶ Alternatively, custom design a modulo N counter as done for BCD

Counting Modulo 7: Detect 7 and Asynchronously Clear

 
- ▶ A synchronous 4-bit binary counter with an asynchronous Clear is used to make a Modulo 7 counter.
- ▶ Use the Clear feature to detect the count 7 and clear the count to 0. This gives a count of 0, 1, 2, 3, 4, 5, 6, 7(short)0, 1, 2, 3, 4, 5, 6, 7(short)0, etc.



- **DON'T DO THIS!** Existence of state 7 may not be long enough to reliably reset all flip-flops to 0. Referred to as a “suicide” counter! (Count “7” is “killed,” but the designer’s job may be dead as well!)

Counting Modulo 7: Synchronously Load on Terminal Count of 6

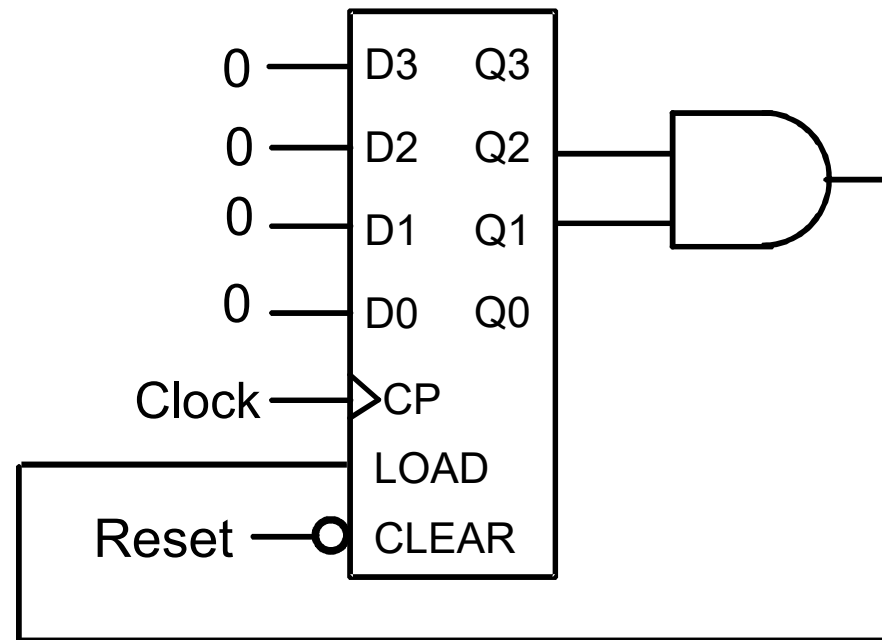
- ▶ A synchronous 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a Modulo 7 counter
- ▶ Use the Load feature to detect the count "6" and load in "zero". This gives a count of 0, 1, 2, 3, 4, 5, 6, 0, 1, 2, 3, 4, 5, 6, 0, ...
- ▶ Using don't cares for states above 0110, detection of 6 can be done with $\text{Load} = Q_2 Q_1$



Counting Modulo 6: Synchronously Preset 9 on Reset and Load 9 on Terminal Count 14

- ▶ A synchronous, 4-bit binary counter with a synchronous Load is to be used to make a Modulo 6 counter.

 - ▶ Use the Load feature to preset the count to 9 on Reset and detection of count 14.



- ▶ This gives a count of 9, 10, 11, 12, 13, 14, 9, 10, 11, 12, 13, 14, 9, ...
- ▶ If the terminal count is 15 detection is usually built in as Carry Out (CO)

Counter Design Example

- ▶ Design a counter to repeat sequence of six states as in table

State Table and Flip-Flop Inputs for Counter

| Present State | | | Next State | | |
|---------------|---|---|-------------|-------------|-------------|
| A | B | C | DA = A(t+1) | DB = B(t+1) | DC = C(t+1) |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |

Counter Design Example

- Design a counter to repeat sequence of six states as in table

State Table and Flip-Flop Inputs for Counter



| Present State | | | Next State | | |
|---------------|---|---|-------------|-------------|-------------|
| A | B | C | DA = A(t+1) | DB = B(t+1) | DC = C(t+1) |
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |

$$DA = A \oplus B$$

$$DB = C$$

$$DC = \overline{B} \overline{C}$$

Counter Design Example

 
 


Counter Design Example 2

- ▶ Using D flip flops and gates design a binary counter to repeat sequence of states 1, 2, 6

Counter Design Example 3

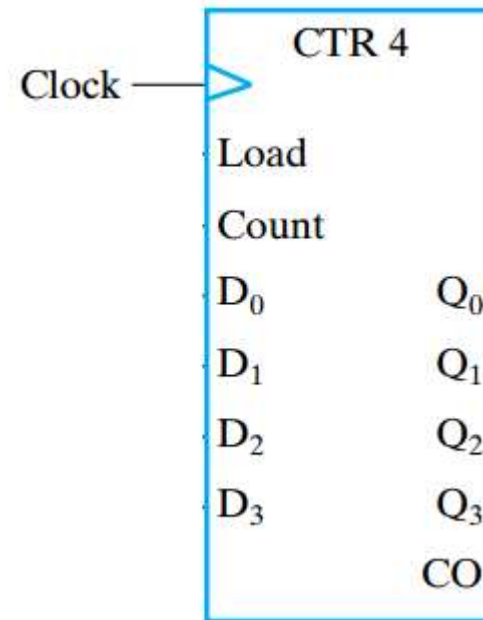 - Using synchronous binary counter and an AND gate construct a counter that counts from 0000 through 0101



Any Questions?

