

ROBT206 – Microcontrollers with Lab

Lecture 10 – Combinational Logic Design

8 February, 2018

Course Logistics

Important Dates and Tasks

Reading Assignment: Mano Chapters 3 and 4

Quiz #2 on 15 February: Till the end of Other gates lecture

Midterm exam on 22 Feb : Mano Chapters 1-4 (till the end of combinational logic)

Topics

Today's Topics

Design Procedure for Combinational Logic Design

- Specification
- Formulation
- Optimization

Technology Mapping:

- AND, OR and NOT
- NAND and NOR

Verification: Manual and Simulation


Rudimentary Logic Functions

Decoding

Combinational Circuits

- ▶ A combinational logic circuit has:
 - ▶ A set of m Boolean inputs,
 - ▶ A set of n Boolean outputs, and
 - ▶ n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values

- ▶ A block diagram:

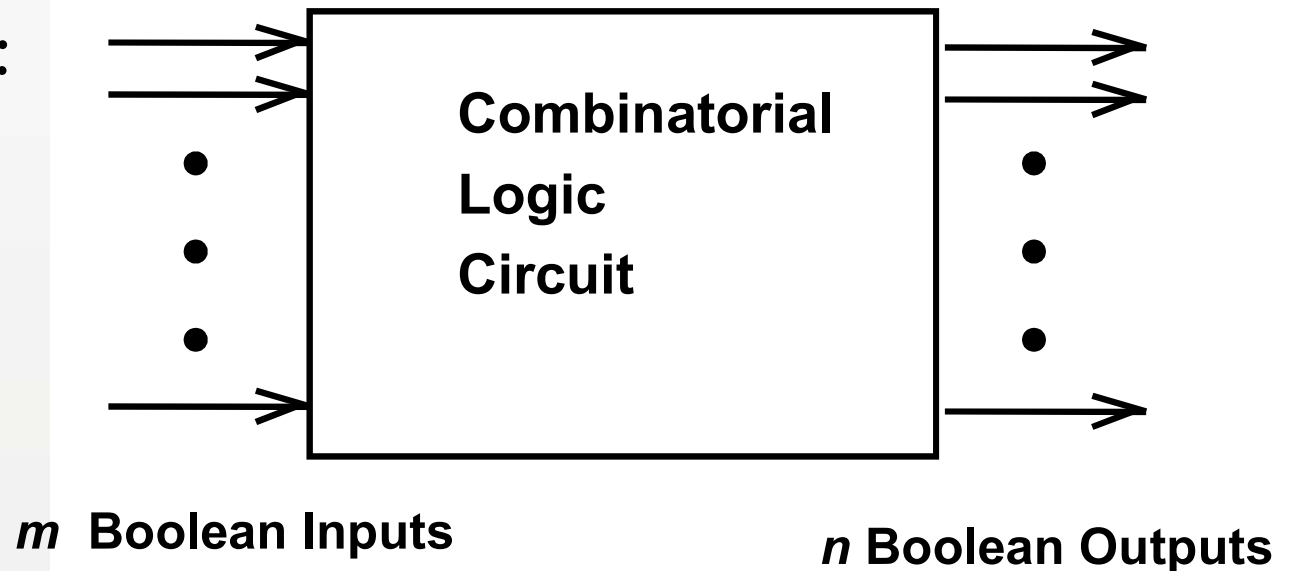

Design Procedure

1. Specification

- ▶ Write a specification for the circuit if one is not already available

2. Formulation

- ▶ Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- ▶ Apply hierarchical design if appropriate

3. Optimization

- ▶ Apply 2-level and multiple-level optimization
- ▶ Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

Design Procedure

4. Technology Mapping

- ▶ Map the logic diagram or netlist to the implementation technology selected

5. Verification

- ▶ Verify the correctness of the final design manually or using simulation

Design Example

I. Specification

- ▶ BCD to Excess-3 code converter
- ▶ Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- ▶ BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- ▶ Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- ▶ Implementation:
 - ▶ multiple-level circuit
 - ▶ AND, OR and NOT gates

Design Example (Continued)

2. Formulation

- ▶ Conversion of 4-bit codes can be most easily formulated by a truth table

- ▶ Variables

- BCD:

- A,B,C,D

- ▶ Variables

- Excess-3

- W,X,Y,Z

- ▶ Don't Cares

- BCD 1010

- to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

Design Example (Continued)

3. Optimization





2-level using K-maps

$$W = A + BC + BD$$

$$X = \bar{B}D + \bar{B}C + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

    

Design Example (Continued)

3. Optimization (continued)

- ▶ Multiple-level using transformations

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

- ▶ Perform extraction, finding factor:

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \bar{B}T_1 + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$

$$Z = \bar{D}$$

Design Example (Continued)

3. Optimization (continued)

- ▶ Multiple-level using transformations

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

- ▶ An additional extraction not shown in the text since it uses a Boolean transformation: ($\overline{C}\overline{D} = \overline{C + D} = \overline{T_1}$):

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{T_1}$$


$$Y = CD + \overline{T_1}$$

$$Z = \overline{D}$$

Design Example (Continued)

 4. Technology Mapping

Mapping with a library containing inverters, 2-input AND and OR gates




Beginning Hierarchical Design


- ▶ To control the complexity of the function mapping inputs to outputs:
 - ▶ Decompose the function into smaller pieces called *blocks*
 - ▶ Decompose each block's function into smaller blocks, repeating as necessary until all blocks are small enough
 - ▶ Any block not decomposed is called a *primitive block*
 - ▶ The collection of all blocks including the decomposed ones is a *hierarchy*
- ▶ Example: 9-input parity tree (see next slide)
 - ▶ Top Level: 9 inputs, one output
 - ▶ 2nd Level: Four 3-bit odd parity trees in two levels
 - ▶ 3rd Level: Two 2-bit exclusive-OR functions
 - ▶ Primitives: Four 2-input NAND gates
 - ▶ Design requires $4 \times 2 \times 4 = 32$ 2-input NAND gates

Hierarchy for Parity Tree Example


(a) Symbol for circuit

 

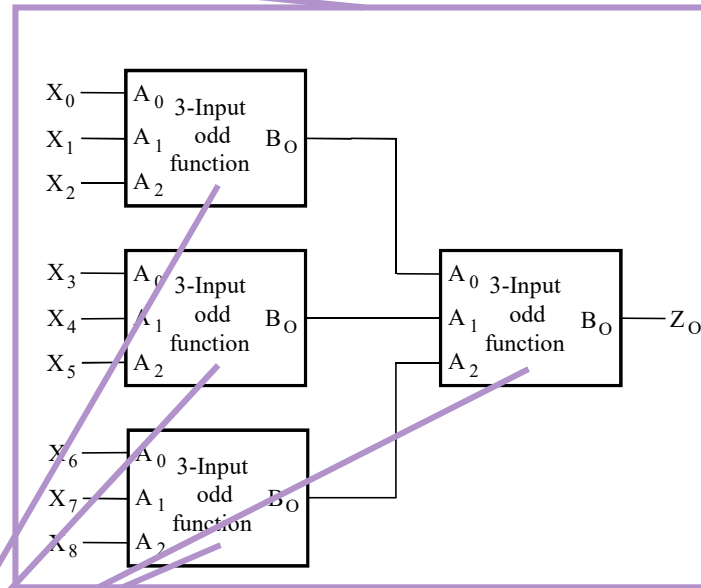
(b) Circuit as interconnected 3-input odd function blocks



 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



 (d) Exclusive-OR block as interconnected NANDs



Reusable Functions

- ▶ Whenever possible, we try to decompose a complex design into common, *reusable* function blocks
- ▶ These blocks are
 - ▶ verified and well-documented
 - ▶ placed in libraries for future use

Top-Down versus Bottom-Up

- ▶ A **top-down design** proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement
- ▶ A **bottom-up design** starts with detailed primitive blocks and combines them into larger and more complex functional blocks
- ▶ Design usually proceeds top-down to known building blocks ranging from complete CPUs to primitive logic gates or electronic components.
- ▶ Much of the material devoted to learning about combinational blocks uses the top-down design.

Technology Mapping



- ▶ Mapping Procedures
 - ▶ To NAND gates
 - ▶ To NOR gates

Mapping to NAND gates

- ▶ Assumptions:
 - ▶ Gate loading and delay are ignored
 - ▶ Cell library contains an inverter and n -input NAND gates, $n = 2, 3, \dots$
 - ▶ An AND, OR, inverter schematic for the circuit is available
- ▶ The mapping is accomplished by:
 - ▶ Replacing AND and OR symbols,
 - ▶ Pushing inverters through circuit fan-out points, and
 - ▶ Canceling inverter pairs

NAND Mapping Algorithm


1. Replace ANDs and ORs:

  


2. Repeat the following pair of actions until there is at most one inverter between:

- a. A circuit input or driving NAND gate output, and


- b. The attached NAND gate inputs.

 


NAND Mapping Example

 


(a)

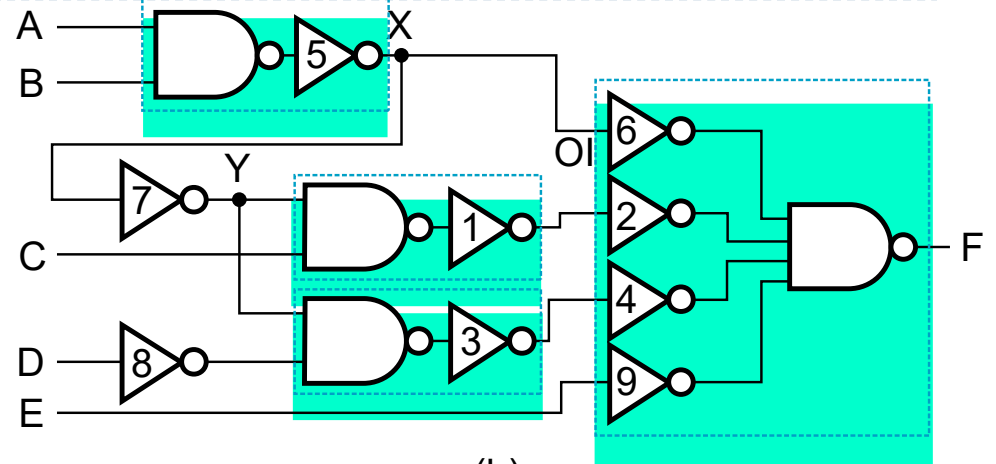

(b)

 

(c)

 


(d)

Mapping to NOR gates

- ▶ Assumptions:
 - ▶ Gate loading and delay are ignored
 - ▶ Cell library contains an inverter and n -input NOR gates, $n = 2, 3, \dots$
 - ▶ An AND, OR, inverter schematic for the circuit is available
- ▶ The mapping is accomplished by:
 - ▶ Replacing AND and OR symbols,
 - ▶ Pushing inverters through circuit fan-out points, and
 - ▶ Canceling inverter pairs


NOR Mapping Algorithm

1. Replace ANDs and ORs:



 


2. Repeat the following pair of actions until there is at most one inverter between :

 - a. A circuit input or driving NAND gate output, and
- b. The attached NAND gate inputs.



NOR Mapping Example

   

Verification

- ▶ Verification - show that the final circuit designed implements the original specification
- ▶ Simple specifications are:
 - ▶ truth tables
 - ▶ Boolean equations
 - ▶ HDL code
- ▶ If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!

Basic Verification Methods

▶ Manual Logic Analysis

- ▶ Find the truth table or Boolean equations for the final circuit
- ▶ Compare the final circuit truth table with the specified truth table, or
- ▶ Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

▶ Simulation

- ▶ Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- ▶ The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification

Verification Example: Manual Analysis

- Find the circuit truth table from the equations and compare to specification truth table:

Input BCD A B C D	Output Excess3- WXYZ
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 0 1 1


The tables match!

Verification Example: Simulation

- ▶ Simulation procedure:
 - ▶ Use a schematic editor or text editor to enter a gate level representation of the final circuit
 - ▶ Use a waveform editor or text editor to enter a test consisting of a sequence of input combinations to be applied to the circuit
 - ▶ This test should guarantee the correctness of the circuit if the simulated responses to it are correct
 - ▶ Short of applying all possible “care” input combinations, generation of such a test can be difficult

Verification Example: Simulation

 
- ▶ Enter waveform that applies all possible input combinations:



- ▶ Are all BCD input combinations present? (Low is a 0 and high is a one)

Verification Example: Simulation

 - ▶ Run the simulation of the circuit for 120 ns



Rudimentary Logic Functions

- Functions of a single variable X
- Can be used on the inputs to functional blocks to implement other than the block's intended function

□ **TABLE 4-1**
Functions of One Variable

X	$F = 0$	$F = X$	$F = \bar{X}$	$F = 1$
0	0	0	1	1
1	0	1	0	1

1 $F = 1$

0 $F = 0$

(a)

V_{CC} or V_{DD}

$F = 1$ X $F = X$

(c)




$F = 0$

X $F = \bar{X}$


(d)

Multiple-bit Functions


Multi-bit Examples:

 


(a)

 

(b)

 

(c)

 


(d)

- ▶ A wide line is used to represent a *bus* which is a vector signal
- ▶ In (b) of the example, $F = (F_3, F_2, F_1, F_0)$ is a bus.
- ▶ The bus can be split into individual bits as shown in (b)
- ▶ Sets of bits can be split from the bus as shown in (c) for bits 2 and 1 of F .
- ▶ The sets of bits need not be continuous as shown in (d) for bits 3, 1, and 0 of F .


Enabling Function

- ▶ *Enabling* permits an input signal to pass through to an output
- ▶ *Disabling* blocks an input signal from passing through to an output, replacing it with a fixed value
- ▶ The value on the output when it is disabled can be Hi-Z (as for three-state buffers and transmission gates), 0, or 1

▶ When disabled, 0 output

 

▶ When disabled, 1 output

 


Decoding

- ▶ Decoding – the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- ▶ Circuits that perform decoding are called **decoders**
- ▶ Here, functional blocks for decoding are
 - ▶ called n -to- m line decoders, where $m \leq 2^n$, and
 - ▶ generate 2^n (or fewer) minterms for the n input variables

Decoder Examples

1-to-2-Line Decoder

A	D ₀	D ₁
0	1	0
1	0	1

 


(a)

(b)

2-to-4-Line Decoder

A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

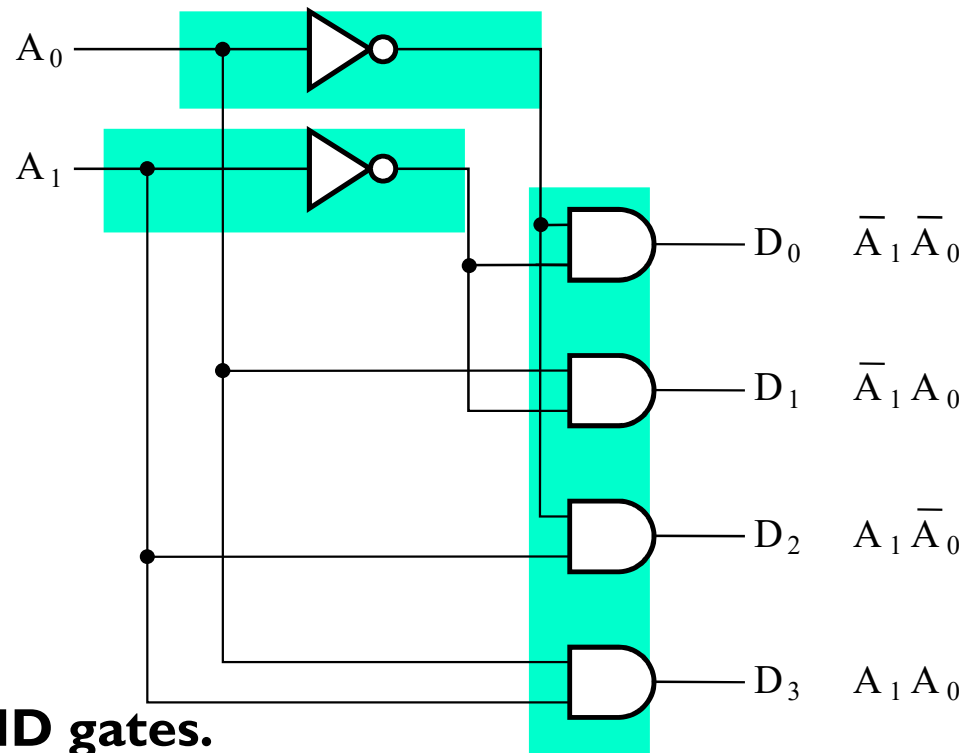

(b)


- Note that the 2-4-line made up of 2 1-to-2-line decoders and 4 AND gates.

Decoder Expansion

- ▶ General procedure given in book for any decoder with n inputs and 2^n outputs.
- ▶ This procedure builds a decoder backward from the outputs.
- ▶ The output AND gates are driven by two decoders with their numbers of inputs either equal or differing by 1.
- ▶ These decoders are then designed using the same procedure until 2-to-1-line decoders are reached.
- ▶ The procedure can be modified to apply to decoders with the number of outputs $\neq 2^n$


Decoder Expansion Example

 - ▶ **3-to-8-line decoder**
 - ▶ Number of output ANDs = 8
 - ▶ Number of inputs to decoders driving output ANDs = 3
 - ▶ Closest possible split to equal
 - ▶ 2-to-4-line decoder
 - ▶ 1-to-2-line decoder
 - ▶ 2-to-4-line decoder
 - ▶ Number of output ANDs = 4
 - ▶ Number of inputs to decoders driving output ANDs = 2
 - ▶ Closest possible split to equal
 - Two 1-to-2-line decoders



Decoder Expansion Example

 Converts n -bit input to m -bit output, where $n \leq m \leq 2^n$




“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Decoder Expansion Example

Converts n-bit input to m-bit output, where $n \leq m \leq 2^n$

e.g., $ABC = 101$ ($i=5$)

 


“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input (ABC)

Decoder Expansion Example

Hierarchical design:

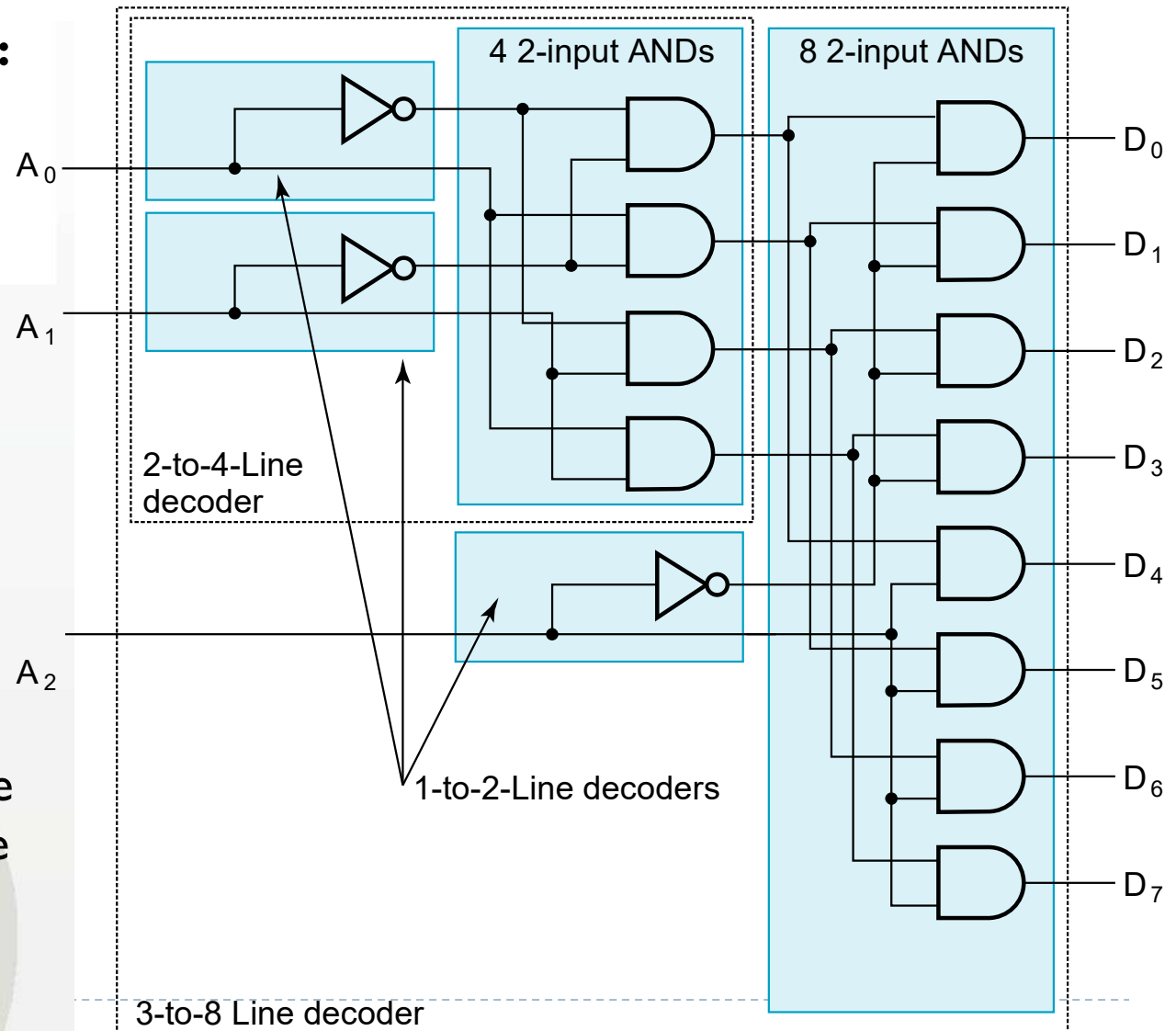
use small decoders to build bigger decoder



Note: A_2 "selects" whether the 2-to-4 line decoder is active in the top half ($A_2=0$) or the bottom ($A_2=1$)

Decoder Expansion Example

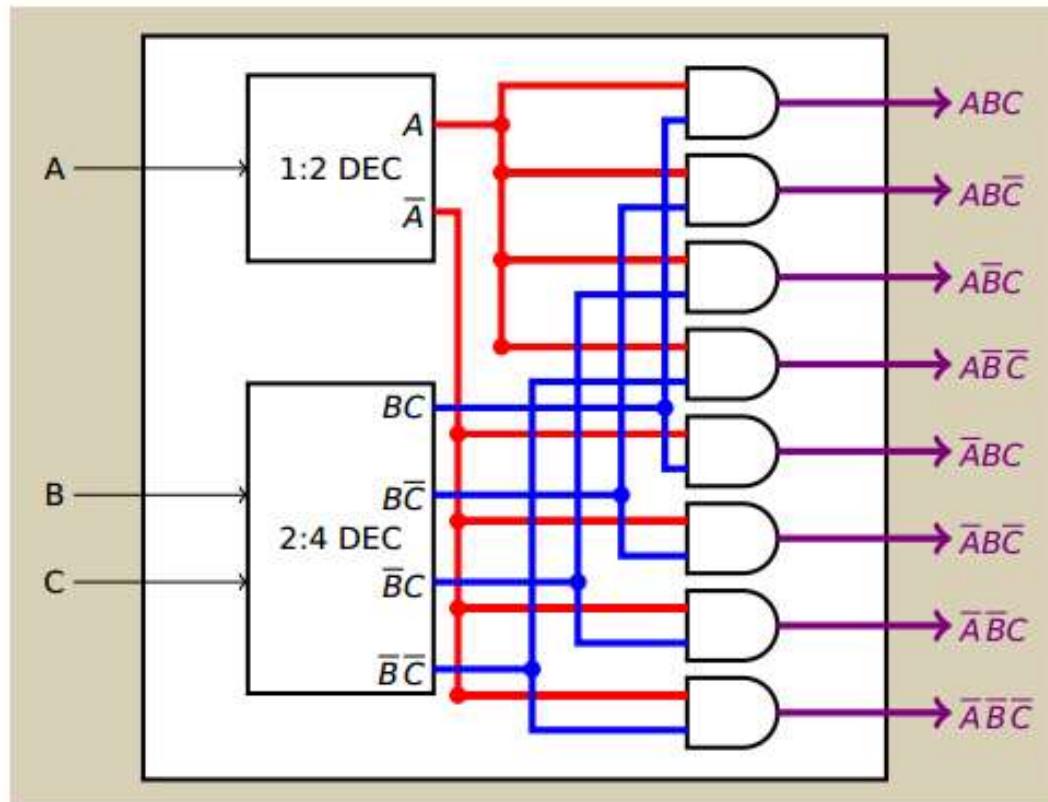Applying *hierarchical design* again, the 2:4 DEC helps construct a 3:8 DEC.




Decoder with Enable

- ▶ In general, attach m -enabling circuits to the outputs
- ▶ See truth table below for function
 - ▶ Note use of X's to denote both 0 and 1
 - ▶ Combination containing two X's represent four binary combinations
- ▶ Alternatively, can be viewed as distributing value of signal EN to 1 of 4 outputs
- ▶ In this case, called a **demultiplexer**

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 

(b)

Combinational Logic Implementation - Decoder and OR Gates

- ▶ Implement m functions of n variables with:
 - ▶ Sum-of-minterms expressions
 - ▶ One n -to- 2^n -line decoder
 - ▶ m OR gates, one for each output
- ▶ Find the minterms for each output function
- ▶ OR the minterms together

Combinational Logic Implementation

Binary Adder Bit Example


- Inputs: Bits X and Y being added with the incoming carry Z from the right
- Outputs: The sum bit S and the carry bit C
- From the truth table, we obtain the functions:

$$S(X,Y,Z) = \sum_m (1,2,4,7)$$

$$C(X,Y,Z) = \sum_m (3,5,6,7)$$

TABLE 3-6
Truth Table for 1-bit Binary Adder

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

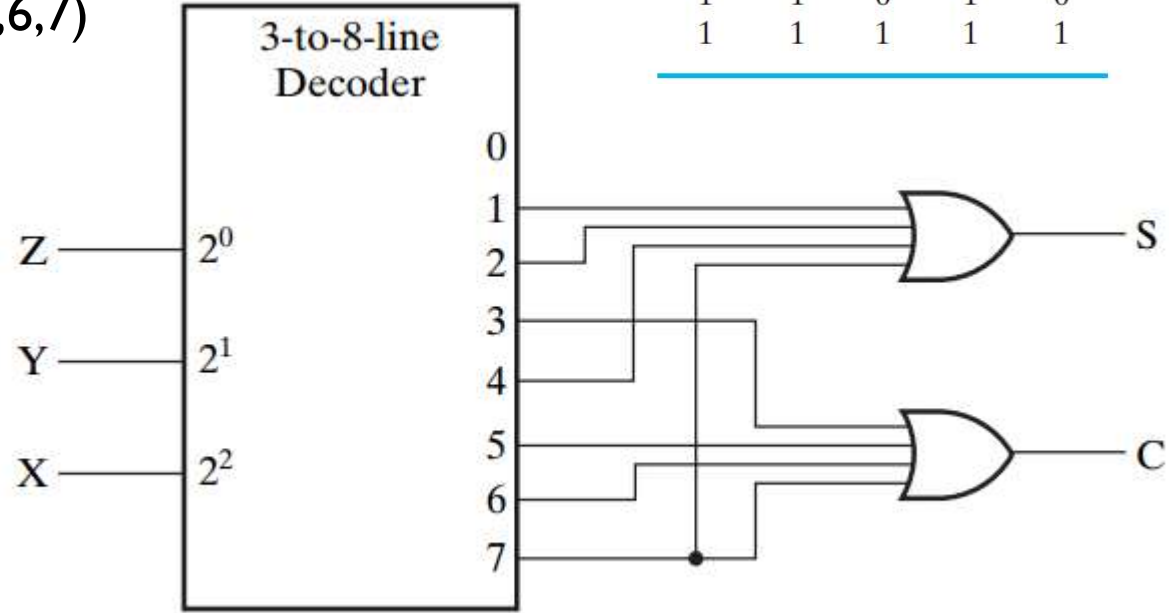


Implementing a Function Using Decoder

Example

E.g., $F = A\bar{C} + BC$

C	B	A	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Warning: Easy, but not a minimal circuit.

Any Questions?

