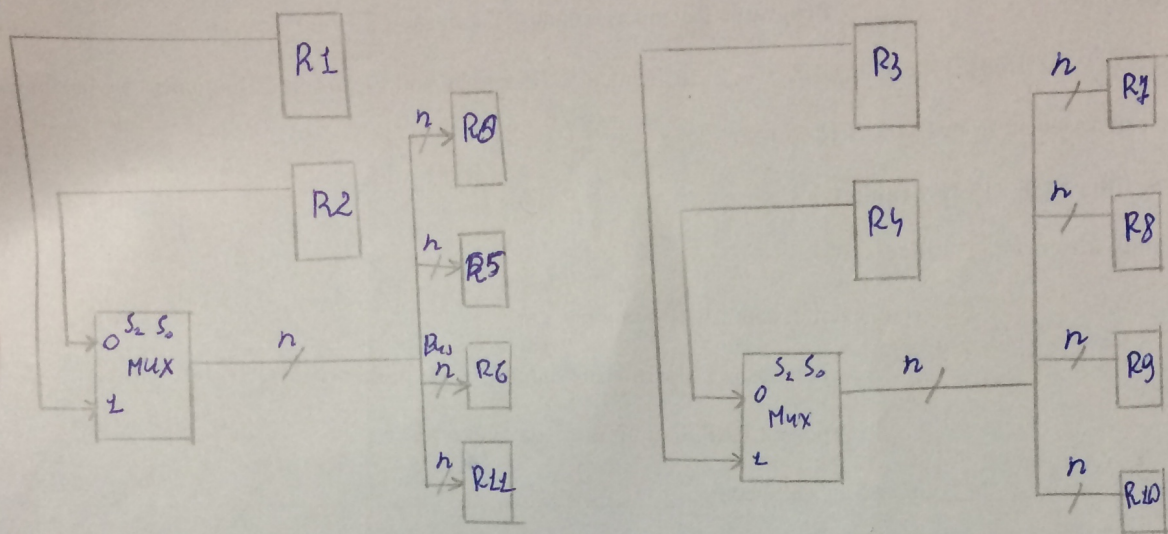


(28) $R_0 \leftarrow R_2$ $R_8 \leftarrow R_3$
 $R_5 \leftarrow R_1$ $R_9 \leftarrow R_4$
 $R_6 \leftarrow R_2$ $R_{10} \leftarrow R_4$
 $R_7 \leftarrow R_3$ $R_{11} \leftarrow R_2$


At most 2 clock cycles
2 buses

b)



(34) State machine: clock CK
 3 external inputs: START, FULL, EMPTY
 External outputs: HOT, COLD, DRAIN, TURN
 Datapath for the control: downcounter which has 3 inputs: RESET, DEC and LOAD and single output: ZERO

a)

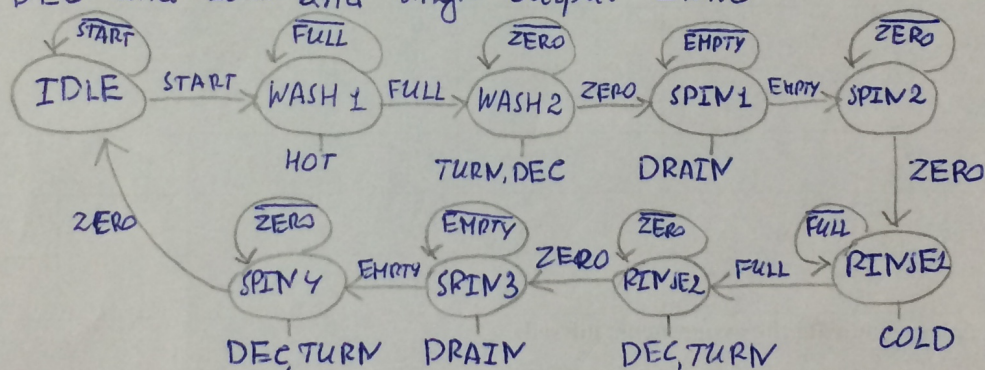

b) 2 more inputs: PAUSE and STOP

Two more states For PAUSE add a FLIP-FLOP set by START and reset by PAUSE. OR Flip-Flop complemented with each input in the loop and AND it with each input on transition.

For STOP a new state: STOP is AND'ed with all input conditions. Each state transitions to state STOP if STOP is 1.

