

ROBT206 – Microcontrollers with Lab

Lecture 13 – Sequential Logic

1 March, 2018

Topics

Today's Topics


Storage Elements and Analysis

- Introduction to sequential circuits
- Types of sequential circuits
- Storage elements
 - Latches
 - Flip-flops

Introduction to Sequential Circuits


- ▶ A Sequential circuit contains:

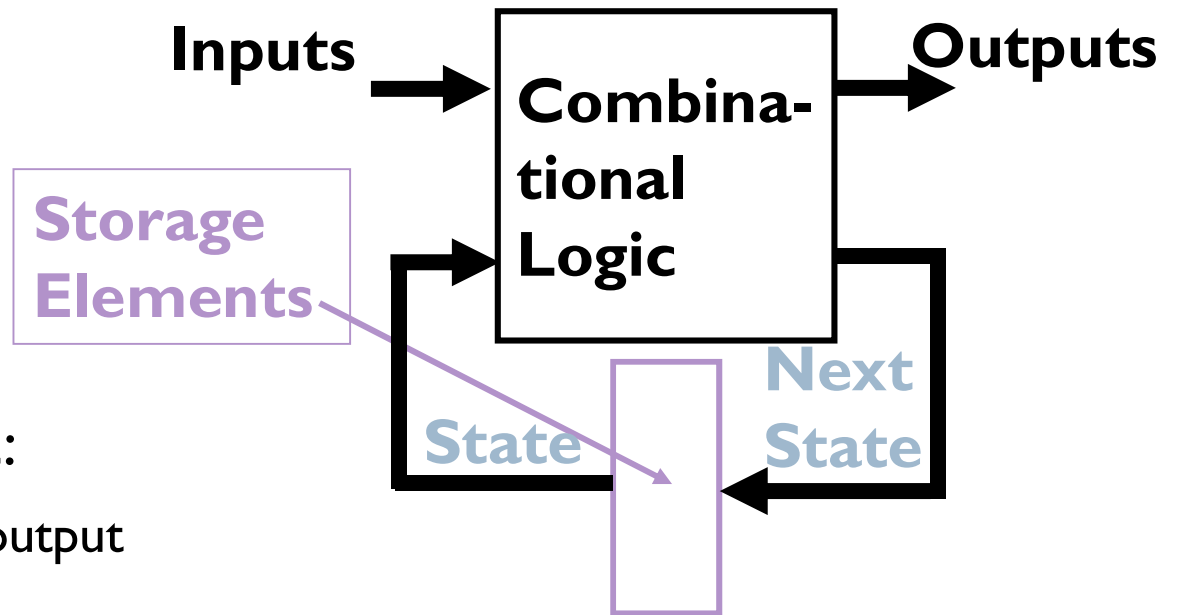- ▶ Storage elements: Latches or Flip-Flops
- ▶ Combinational Logic:
 - ▶ Implements a multiple-output switching function
 - ▶ Inputs are signals from the outside.
 - ▶ Outputs are signals to the outside.
 - ▶ Other inputs, State or Present State, are signals from storage elements.
 - ▶ The remaining outputs, Next State are inputs to storage elements.



Introduction to Sequential Circuits

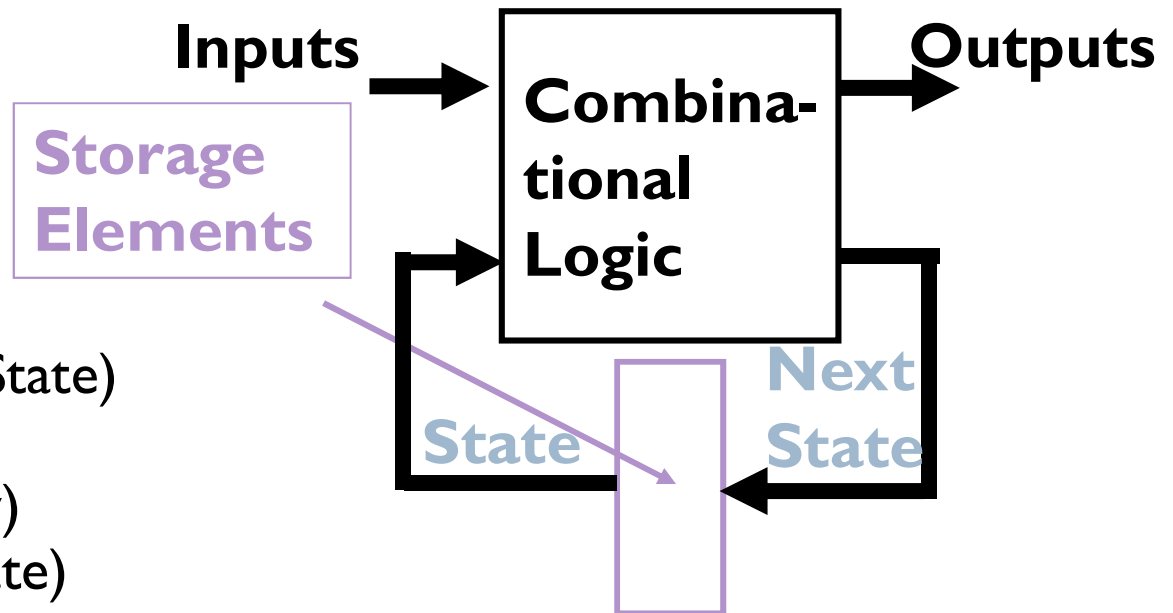- ▶ Combinational Logic
 - ▶ *Next state function*
 $\text{Next State} = f(\text{Inputs}, \text{State})$
 - ▶ *Output function (Mealy)*
 $\text{Outputs} = g(\text{Inputs}, \text{State})$
 - ▶ *Output function (Moore)*
 $\text{Outputs} = h(\text{State})$
- ▶ Output function type depends on specification and affects the design significantly



Types of Sequential Circuits


- ▶ Depends on the times at which:
 - ▶ storage elements observe their inputs, and
 - ▶ storage elements change their state
 - ▶ **Synchronous**
 - ▶ Behavior defined from knowledge of its signals at discrete instances of time
 - ▶ Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
 - ▶ **Asynchronous**
 - ▶ Behavior defined from knowledge of inputs at any instant of time and the order in continuous time in which inputs change
 - ▶ If clock just regarded as another input, all circuits are asynchronous!
 - ▶ Nevertheless, the synchronous abstraction makes complex designs tractable!
-

Discrete Event Simulation

- ▶ In order to understand the time behavior of a sequential circuit we use discrete event simulation.
- ▶ Rules:
 - ▶ Gates modeled by an ideal (instantaneous) function and a fixed gate delay
 - ▶ Any change in input values is evaluated to see if it causes a change in output value
 - ▶ Changes in output values are scheduled for the fixed gate delay after the input change
 - ▶ At the time for a scheduled output change, the output value is changed along with any inputs it drives

Simulated NAND Gate

 - ▶ Example: A 2-Input NAND gate with a 0.5 ns. delay:





- ▶ Assume A and B have been 1 for a long time
- ▶ At time $t=0$, A changes to a 0 at $t=0.8$ ns, back to 1.

t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	A=B=1 for a long time
0	$1 \Rightarrow 0$	1	$1 \Leftarrow 0$	0	F(I) changes to 1
0.5	0	1	1	$1 \Leftarrow 0$	F changes to 1 after a 0.5 ns delay
0.8	$1 \Leftarrow 0$	1	$1 \Rightarrow 0$	1	F(Instantaneous) changes to 0
0.13	1	1	0	$1 \Rightarrow 0$	F changes to 0 after a 0.5 ns delay


Gate Delay Models

  - Suppose gates with delay n ns are represented for $n = 0.2$ ns, $n = 0.4$ ns, $n = 0.5$ ns, respectively:



Circuit Delay Model

 
- ▶ Consider a simple 2-input multiplexer:
- ▶ With function:
 - ▶ $Y = A$ for $S = 0$
 - ▶ $Y = B$ for $S = 1$




- “Glitch” is due to delay of inverter

Basic (NOR) S – R Latch

 - ▶ Cross-coupling two NOR gates gives the S – R Latch:
- ▶ Which has the time sequence behavior:




Basic (NOR) S – R Latch

 


R	S	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Basic (NOR) S – R Latch

 


R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set ($Q = 1$)
1	0			
1	1			

Basic (NOR) S – R Latch

 


R	S	Q	\bar{Q}	
0	0			
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			

Basic (NOR) S – R Latch

 

R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1			


Basic (NOR) S – R Latch

 

R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	Hold previous value
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
1	1	0	0	Bad. Do not use.

Basic (NAND) \bar{S} - \bar{R} Latch

 - ▶ “Cross-Coupling”
two NAND gates
gives \bar{S} - \bar{R} latch:
- ▶ Which has the time
sequence behavior:




- ▶ $S = 0, R = 0$
is forbidden as
input pattern

\bar{R}	\bar{S}	Q	\bar{Q}	
0	0	1	1	Bad. Do not use.
0	1	0	1	Reset ($Q = 0$)
1	0	1	0	Set ($Q = 1$)
1	1	Q	\bar{Q}	Hold previous value

Clocked S - R Latch

 - ▶ Adding two NAND gates to the basic \overline{S} - \overline{R} NAND latch gives the clocked S - R latch:




- ▶ Has a time sequence behavior similar to the basic S-R latch except that the S and R inputs are only observed when the line C is high.
- ▶ C means “control” or “clock”.

D Latch


- ▶ Adding an inverter to the S-R Latch, gives the D Latch:
- ▶ Note that there are no “indeterminate” states!

C	D	Q	\overline{Q}
0	X	Q	\overline{Q}
1	0	0	1
1	1	1	0

No change
Reset state
Set state

 

The graphic symbol for a D Latch is:

 

Flip-Flops

- ▶ The latch timing problem
- ▶ Edge-triggered flip-flop
- ▶ Standard symbols for storage elements
- ▶ Direct inputs to flip-flops

The Latch Timing Problem

Latches are circuits that can store “state”

- set the latch to a value (0 or 1)
- put the latch in a “same value” mode to hold the value

To do complicated computations

- intermediate “state” must be maintained
- various steps of the computation must be coordinated

Q: How to coordinate computations and the changing of state values across lots of different parts of a circuit


A: Introduce a clocking mechanism

- each clock pulse, combinational computations can be performed, results stored (in latches)


Q: How to introduce clocks into latches?

The Latch Timing Problem (continued)

- ▶ Consider the following circuit:

 

- ▶ Suppose that initially $Y = 0$.

 


- ▶ As long as $C = 1$, the value of Y continues to change!
- ▶ The changes are based on the delay present on the loop through the connection from Y back to Y .
- ▶ This behavior is clearly unacceptable.
- ▶ Desired behavior: Y changes only once per clock pulse
- ▶ **Flip flops are designed so that outputs will not change within a single clock pulse**

The Latch Timing Problem (continued)



- ▶ A solution to the latch timing problem is to break the closed path from Y to Y within the storage element
- ▶ The commonly-used, path-breaking solutions replace the clocked D-latch with an edge-triggered flip-flop
- ▶ An edge-triggered flip-flop ignores the pulse while it is at a constant level and triggers only during a **transition** of the clock signal
- ▶ Edge-triggered flip-flops can be built directly at the electronic circuit level

Edge-Triggered D Flip-Flop

 


- C (Control) is fed a clock pulse (alternates between 0 and 1 with fixed period)
 - C=1: Master latch “on”, Slave latch “off”
 - New D input read into master
 - Previous Q values still emitted (not affected by new D inputs)
 - C=0: Master latch “off”, Slave latch “on”
 - Changing D inputs has no effect on Master (or Slave) latch
 - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q

Negative-Edge Triggered D Flip-Flop

  




- C=1: Master latch “on”, Slave latch “off”
 - New S & R inputs read into master
 - Previous Q values still emitted (not affected by new S&R inputs)

Negative-Edge Triggered D Flip-Flop

 

- C=0: Master latch “off”, Slave latch “on”
 - Changing D inputs has no effect on Master (or Slave) latch
 - D inputs from last time C=1 stored safely in Master and transferred into Slave and reflected on output Q


D Flip-Flop vs. D Latch

   

Latch outputs change at any time, flip-flops only during clock transitions

Positive-Edge Triggered D Flip-Flop

 - ▶ Formed by adding inverter to clock input




- ▶ Q changes to the value on D applied at the positive clock edge within timing constraints to be specified
- ▶ Our choice as the **standard flip-flop** for most sequential circuits


Standard Symbols for Storage Elements

- Master-Slave:
Postponed output indicators


- Edge-Triggered:
Dynamic indicator

 

(a) Latches

 


(b) Master-Slave Flip-Flops

 

 
(c) Edge-Triggered Flip-Flops

Direct Inputs

- ▶ At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation
- ▶ This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously.
- ▶ Direct R and/or S inputs that control the state of the latches within the flip-flops are used for this initialization.
- ▶ For the example flip-flop shown
 - ▶ 0 applied to \bar{R} resets the flip-flop to the 0 state
 - ▶ 0 applied to \bar{S} sets the flip-flop to the 1 state



 Positive-Edge Triggered D Flip-Flop: Traffic Light Controller



CLK _____



R _____

Y _____


G _____

Initial state: Red light

 
 
Positive-Edge Triggered D Flip-Flop: Traffic Light Controller




 
Positive-Edge Triggered D Flip-Flop: Traffic Light Controller



  Positive-Edge Triggered D Flip-Flop: Traffic Light Controller



  Positive-Edge Triggered D Flip-Flop: Traffic Light Controller



Any Questions?

