



NAZARBAYEV
UNIVERSITY

SCHOOL OF SCIENCE AND TECHNOLOGY

NAME. "Solution" Quiz #3

EXAMINATION RULES

- The duration of this exam is 40 minutes.
- The exam consists of 8 pages including this one. Write your name to each page.
- The total points are 100.
- Students are required to follow all instructions given by the examiners.
- Talking is NOT allowed under any circumstances.
- Students MAY NOT bring any written or printed materials into the examination room except where explicitly allowed by the examiner.
- Mobile phones are strictly prohibited in the examination room.
- Students MAY NOT bring any electronic device into the examination room except where explicitly allowed by the examiner (e.g., calculators with specified capabilities).
- Students may raise their hand to ask the examiner a question. The examiner may decide not to answer the question: students are expected to know the requisite terminology and understand the examination questions.
- For examinations lasting two hours or less, students are NOT allowed to leave the examination room until ready to turn in their work.
- Once a student has seen the examination paper, the student is assumed to be in good health at the time of the examination.

I have read and understood the examination rules. I will not cheat, copy from other students, or use unauthorized materials or devices, and I have not brought such materials or devices into the examination room.

Signed:

Student Name:


ROBT 206 – Microcontrollers with Laboratory Quiz #3

29 March, 2018

Answer ALL the problems. Please provide precise and neat answers.

1. Design a 1-bit width binary full adder with three inputs (X, Y and Z: carry in) and two outputs (C: Carry out and S: Sum). Form and fill a truth table, use K-Map to find optimal expressions for the outputs and implement it. (20 points: 10 points for truth table, 5 points for expressions and 5 points for the implementation)

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

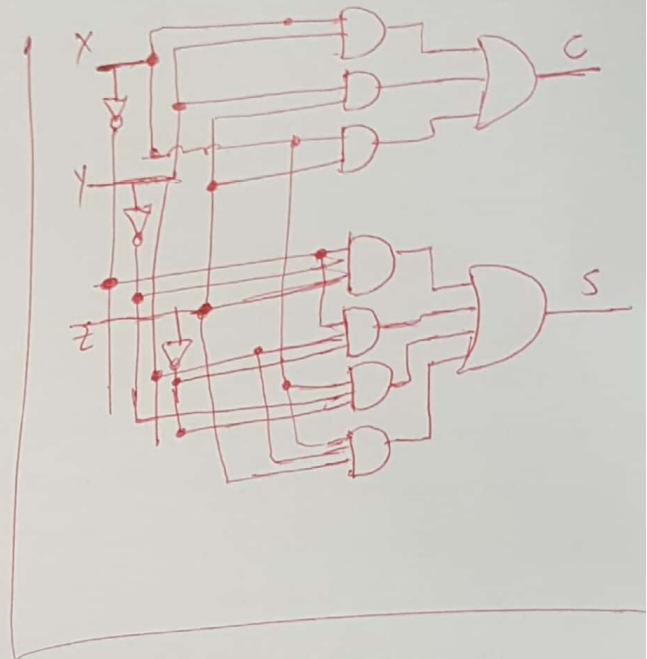

C

X \ YZ	00	01	11	10
0	0	0	1	0
1	0	1	1	1

S

X \ YZ	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$C = YZ + XY + XZ$$

$$S = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

Answer ALL the problems. Please provide precise and neat answers.

2. Find the result of the following subtraction in binary using the 2's complement method (20 points)

a) $(-6)_{10} - (+24)_{10}$

Working with signed numbers, the MSB will be the sign bit. To cover 24 and 6 we would need to have 5 more bits. $\Rightarrow (-6)_{10} = (000110)_2 = (111010)_2$

$$(+24)_{10} = (011000)_2$$

$$\begin{array}{r} 111010 \\ - 011000 \\ \hline \end{array} \Rightarrow \begin{array}{r} 111010 \\ + (011000)' \\ \hline \end{array} \Rightarrow \begin{array}{r} 111010 \\ + 101000 \\ \hline 100010 \end{array}$$

ignore the carry
Negative number

$$(100010)_2 = -(100010)_2' = -(011110)_2 = -(30)_{10}$$

b) $(-3)_{10} - (-12)_{10}$

Similar to part a) \Rightarrow - MSB for sign
- Four more bits to cover 12 and 3 \Rightarrow 5 bits in total

$$(-3)_{10} = (00011)_2 = (11101)_2$$

$$(-12)_{10} = (01100)_2 = (10100)_2$$

$$\Rightarrow \begin{array}{r} 11101 \\ - 10100 \\ \hline \end{array} \equiv \begin{array}{r} 11101 \\ + (10100)' \\ \hline \end{array} \equiv \begin{array}{r} 11101 \\ + 01100 \\ \hline 01001 \end{array}$$

ignore the carry

the actual result is $(01001)_2 = +9_{10}$


Student Name:

ROBT 206 – Microcontrollers with Laboratory Quiz #3

29 March, 2018

Answer ALL the problems. Please provide precise and neat answers.

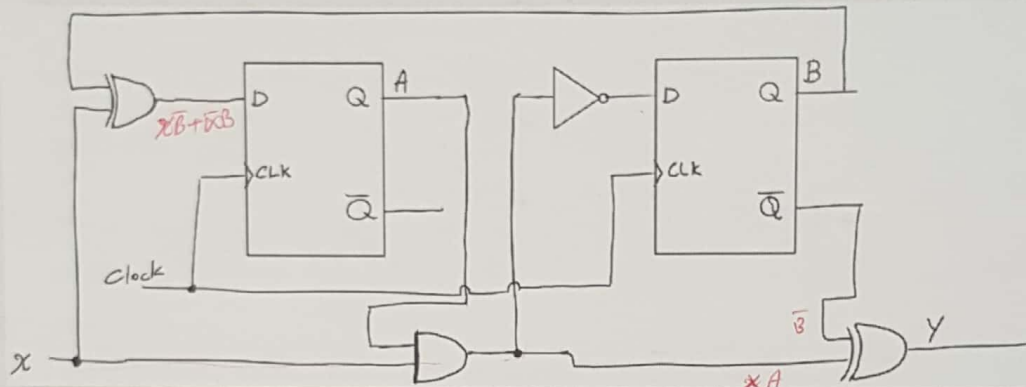3. For the sequential circuit given below, derive the state table, draw the state diagram and find the expressions for the next state and output. Is it a Mealy or a Moore machine (Explain the reason)? (30 points: 10 points for State table, 10 points for state diagram, 5 points for finding expressions, 5 points for Mealy-Moore categorization)



Current State		$x(t)$	Next State		Output $y(t)$
$A(t)$	$B(t)$		$A(t+1)$	$B(t+1)$	
0	0	0	0	1	0 1
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	0	1	1 0
1	0	0	0	1	0 1
1	0	1	1	0	1 0
1	1	0	1	1	0 0
1	1	1	0	0	0 1


Student Name:

ROBT 206 – Microcontrollers with Laboratory Quiz #3

29 March, 2018

Answer ALL the problems. Please provide precise and neat answers.

State diagram

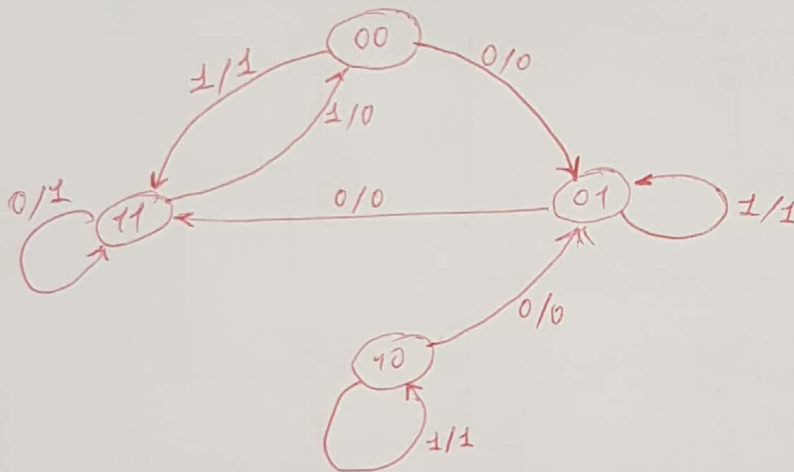

$$A(t+1) = B(t) \oplus X(t)$$


$$B(t+1) = \overline{A(t) \cdot X(t)}$$

$$Y(t) = (X(t) \cdot A(t+1)) \oplus \overline{B(t)}$$

It is a Mealy machine, as the outputs depends on state & input.

Answer ALL the problems. Please provide precise and neat answers.

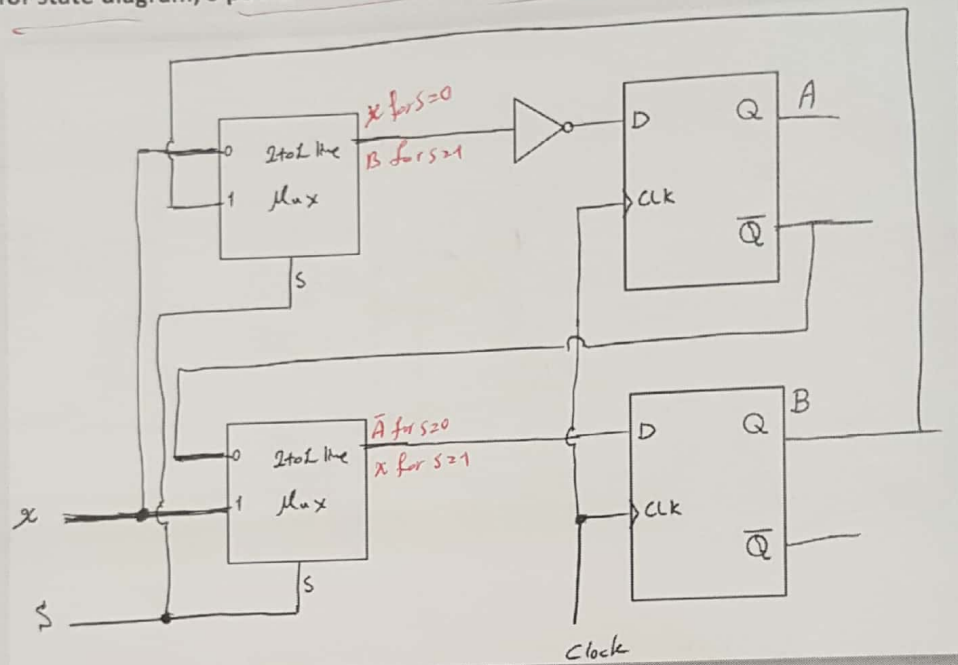4. For the sequential circuit given below, derive the state table, draw the state diagram, find the expressions for next states, and re-implement it without using multiplexers. (30 points: 10 points for State table, 10 points for state diagram, 5 points for finding the expressions and 5 points for implementation)



State Table

Current State		inputs		Next State	
A(t)	B(t)	X	S	A(t+1)	B(t+1)
0	0	0	0	$\bar{x} = 1$	$\bar{A} = 1$
0	0	0	1	$\bar{B} = 1$	$x = 0$
0	0	1	0	$\bar{x} = 0$	$\bar{A} = 1$
0	0	1	1	$\bar{B} = 1$	$x = 1$
0	1	0	0	$\bar{x} = 1$	$\bar{A} = 1$
0	1	0	1	$\bar{B} = 0$	$x = 0$
0	1	1	0	$\bar{x} = 0$	$\bar{A} = 1$
0	1	1	1	$\bar{B} = 0$	$x = 1$
1	0	0	0	$\bar{x} = 1$	$\bar{A} = 0$
1	0	0	1	$\bar{B} = 1$	$x = 0$
1	0	1	0	$\bar{x} = 0$	$\bar{A} = 0$
1	0	1	1	$\bar{B} = 1$	$x = 1$
1	1	0	0	$\bar{x} = 1$	$\bar{A} = 0$
1	1	0	1	$\bar{B} = 0$	$x = 0$
1	1	1	0	$\bar{x} = 0$	$\bar{A} = 0$
1	1	1	1	$\bar{B} = 0$	$x = 1$


Student Name:

ROBT 206 – Microcontrollers with Laboratory Quiz #3

29 March, 2018

Answer ALL the problems. Please provide precise and neat answers.

State diagram

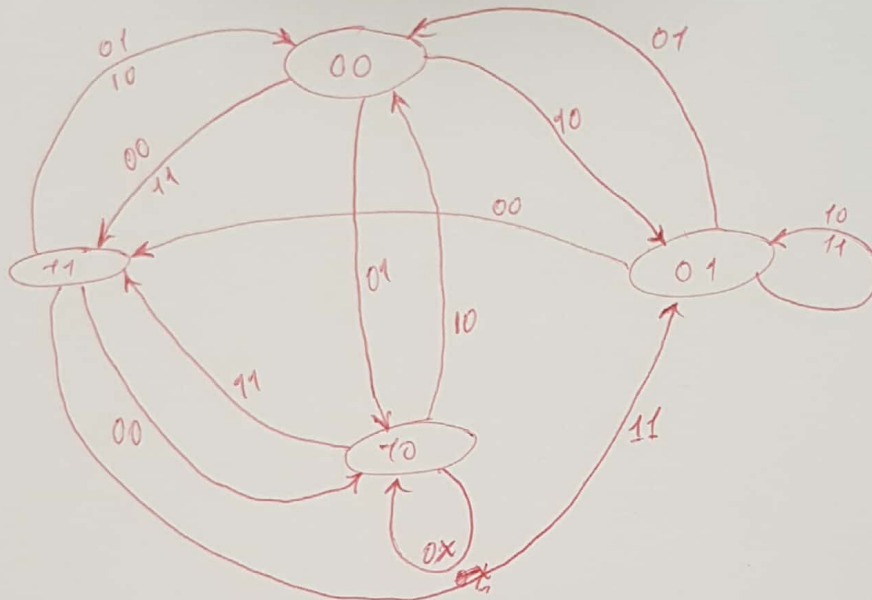

$$A(t+1) = D_A(t) = \bar{X}\bar{S} + \bar{B}S$$

$$B(t+1) = D_B(t) = \bar{A}(t) \cdot \bar{S} + X \cdot S$$

DA

XS \ AB	00	01	10	11
00	1	1	1	0
01	1	0	0	0
10	1	0	0	0
11	1	1	1	0

DB

XS \ AB	00	01	10	11
00	1	0	1	1
01	1	0	1	1
10	0	0	1	0
11	0	0	1	0

