

ROBT206 – Microcontrollers with Lab

Lecture 14 – Sequential Circuit Analysis

6 March, 2018

Topics

Today's Topics

- Sequential circuit analysis
 - State tables
 - State diagrams
 - Equivalent states
 - Moore and Mealy Models


Sequential Circuit Analysis

▶ General Model

- ▶ Current State at time (t) is stored in an array of flip-flops.

- ▶ Next State at time $(t+1)$ is a Boolean function of state and inputs.

- ▶ Outputs at time (t) are a Boolean function of State (t) and (sometimes) Inputs (t) .

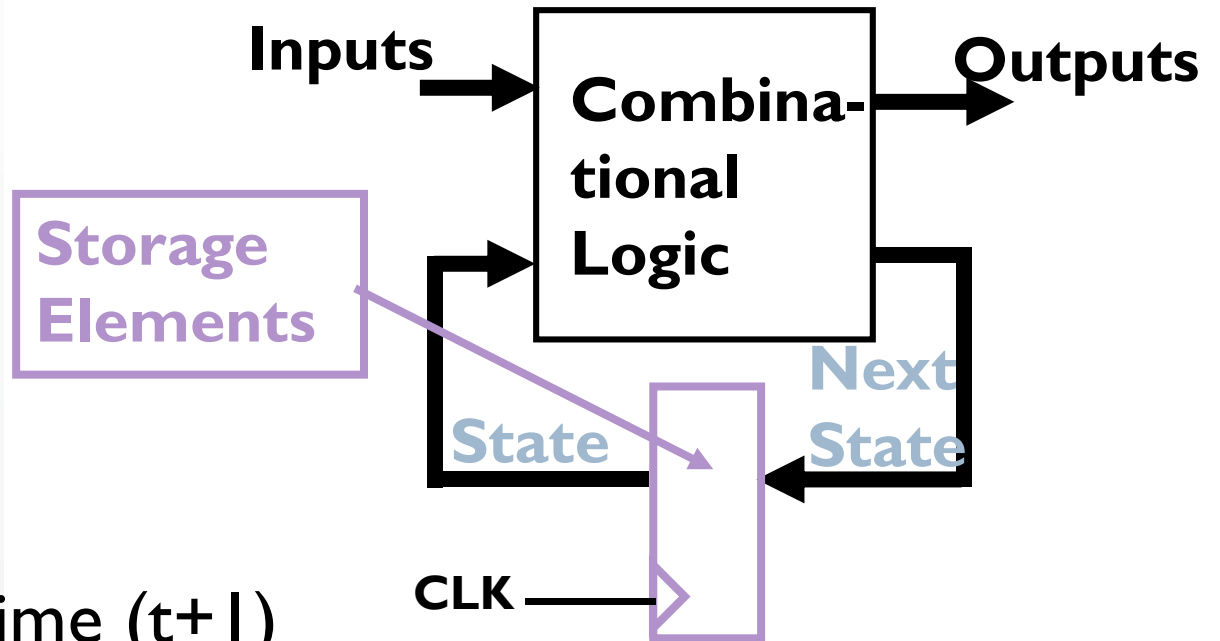


Example 1

- ▶ Input: $x(t)$
- ▶ Output: $y(t)$
- ▶ State: $(A(t), B(t))$

▶ What is the Output Function?

- ▶ What is the
- ▶ Next State Function?

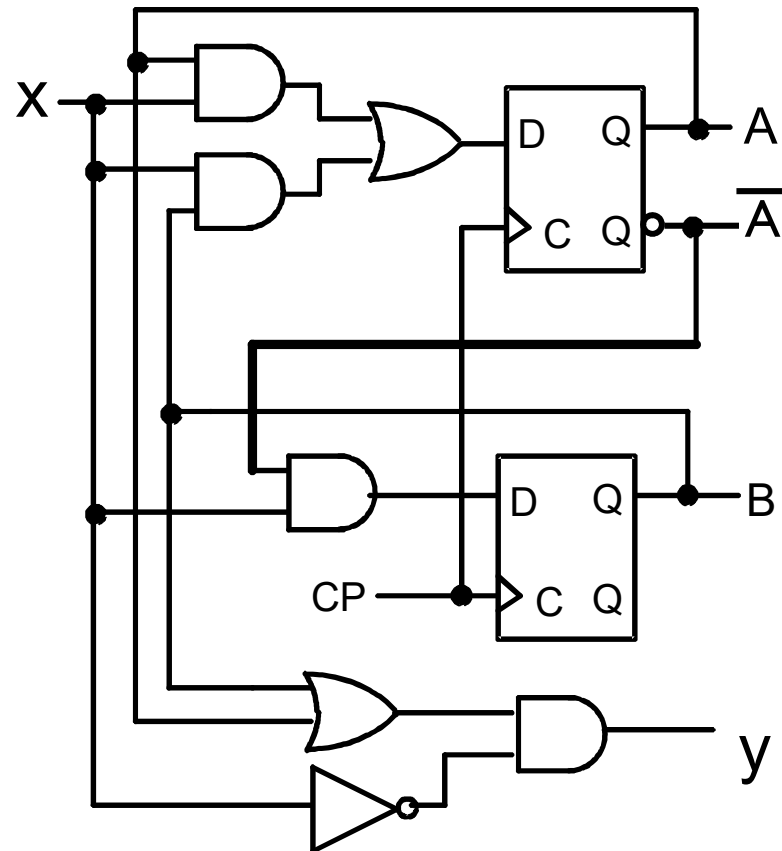


Example 1 (continued)

- ▶ Boolean equations for the functions:

- ▶ $A(t+1) = A(t)x(t) + B(t)x(t)$

- ▶ $B(t+1) = \bar{A}(t)x(t)$


- ▶ $y(t) = \bar{x}(t)(B(t) + A(t))$

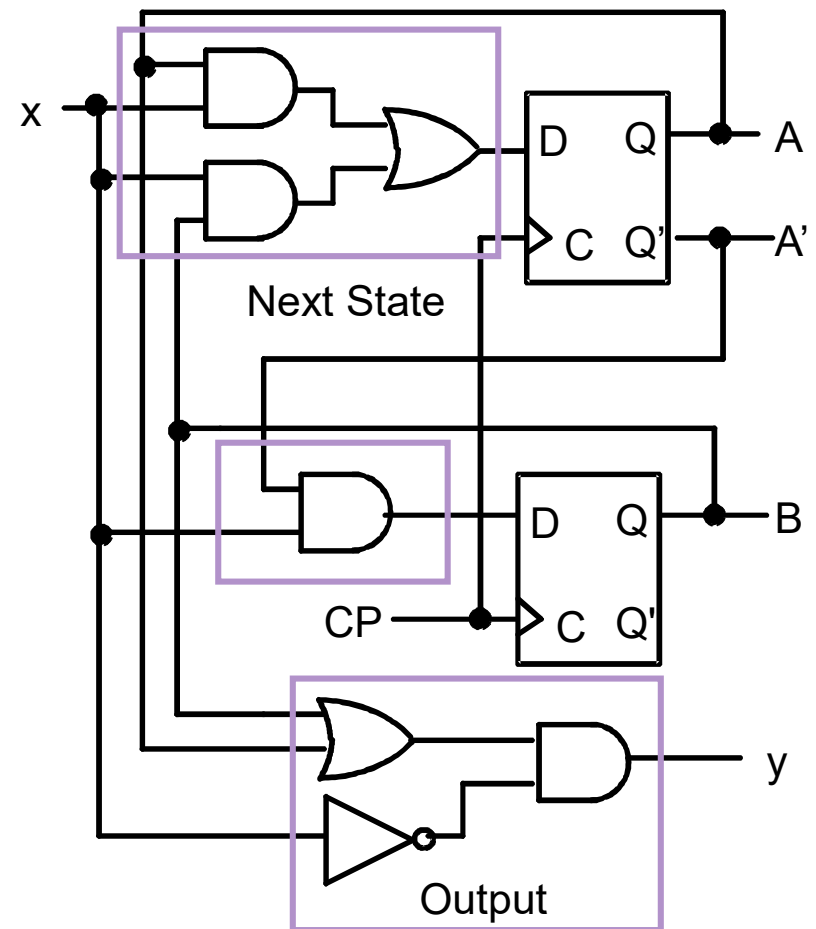

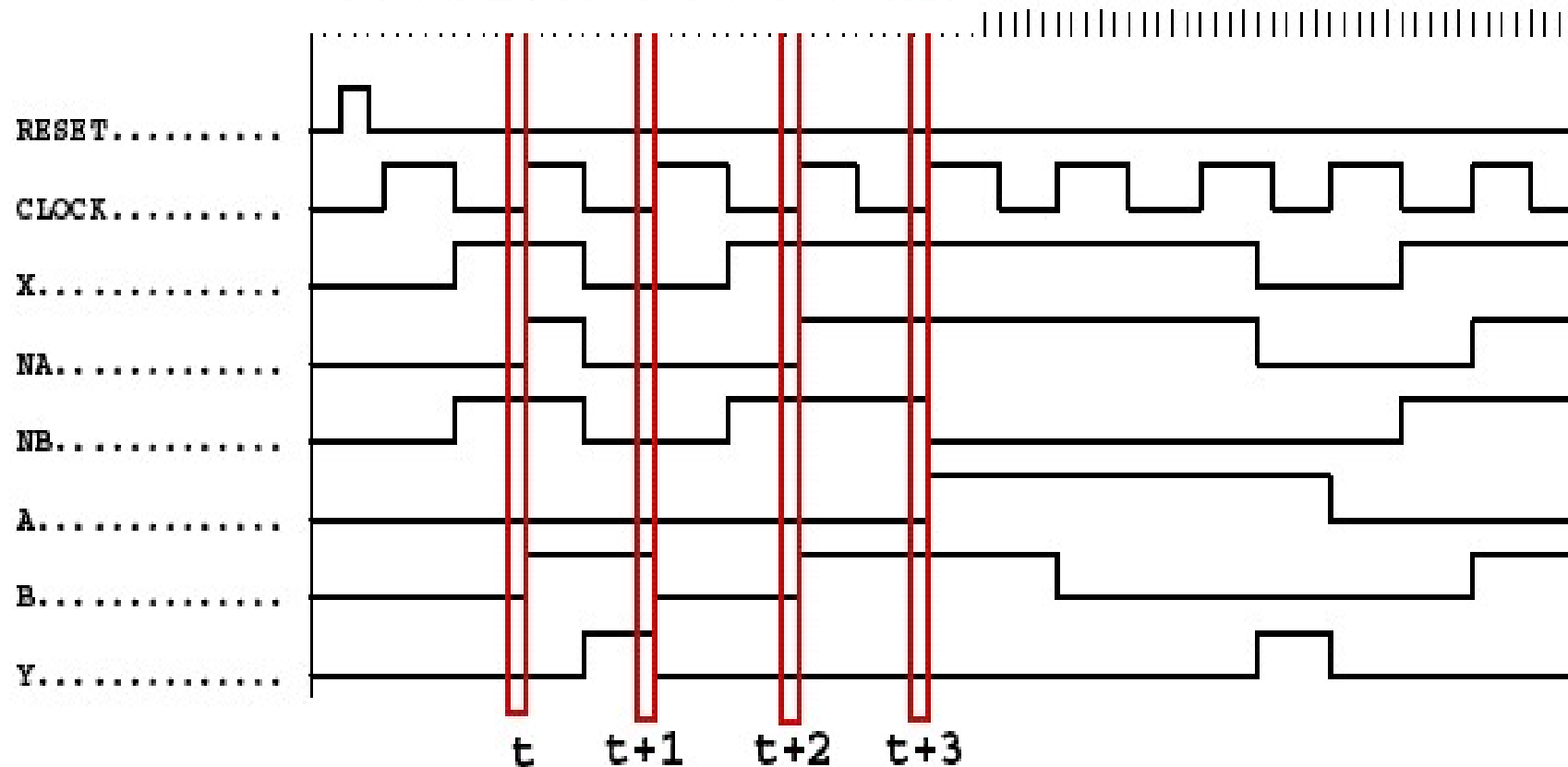Example 1 (continued)

- Where in time are inputs, outputs and states defined?

Functional Simulation - Fig. 4-18 Mano & Kime



State Table Characteristics

- ▶ *State table* – a multiple variable table with the following four sections:
 - ▶ **Present State** – the values of the state variables for each allowed state.
 - ▶ **Input** – the input combinations allowed.
 - ▶ **Next-state** – the value of the state at time $(t+1)$ based on the present state and the input.
 - ▶ **Output** – the value of the output as a function of the present state and (sometimes) the input.
- ▶ From the viewpoint of a truth table:
 - ▶ the inputs are Input, Present State
 - ▶ and the outputs are Output, Next State

Example 1: State Table

- ▶ The state table can be filled in using the next state and output equations:

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \bar{A}(t)x(t)$$

$$y(t) = \bar{x}(t)(B(t) + A(t))$$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Example 1: Alternate State Table

- ▶ 2-dimensional table that matches well to a K-map. Present state rows and input columns in Gray code order.
 - ▶ $A(t+1) = A(t)x(t) + B(t)x(t)$
 - ▶ $B(t+1) = \bar{A}(t)x(t)$
 - ▶ $y(t) = \bar{x}(t)(B(t) + A(t))$

Present State A(t) B(t)	Next State		Output	
	x(t)=0 A(t+1)B(t+1)	x(t)=1 A(t+1)B(t+1)	x(t)=0 y(t)	x(t)=1 y(t)
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

State Diagrams


- ▶ The sequential circuit function can be represented in graphical form as a state diagram with the following components:
 - ▶ A circle with the state name in it for each state
 - ▶ A directed arc from the Present State to the Next State for each state transition
 - ▶ A label on each directed arc with the Input values which causes the state transition, and
 - ▶ A label:
 - ▶ On each circle with the output value produced, or
 - ▶ On each directed arc with the output value produced.

State Diagrams

- ▶ Label form:
 - ▶ On circle with output included:
 - ▶ state/output
 - ▶ Moore type output depends only on state
 - ▶ On directed arc with the output included:
 - ▶ input/output
 - ▶ Mealy type output depends on state and input

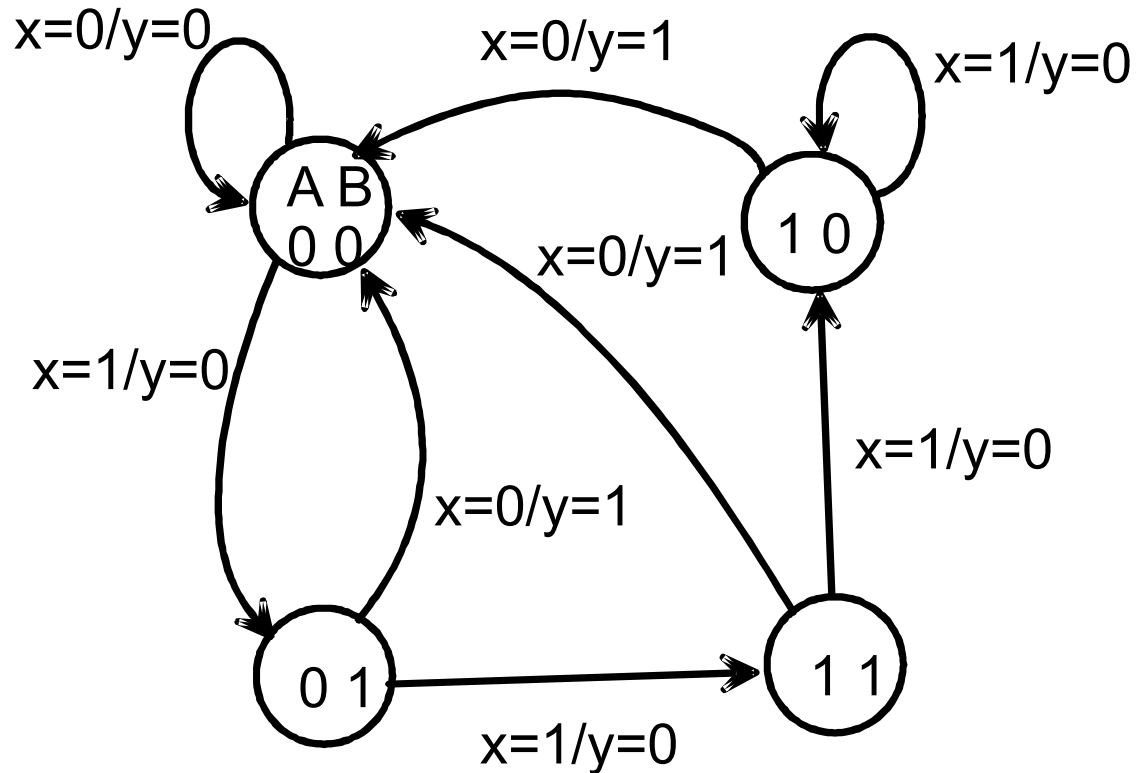Example 1: State Diagram

- ▶ Which type?
- ▶ Diagram gets confusing for large circuits
- ▶ For small circuits, usually easier to understand than the state table



Moore and Mealy Models

- ▶ Sequential Circuits or Sequential Machines are also called ***Finite State Machines*** (FSMs). Two formal models exist:

- Moore Model


- Named after E.F. Moore
- Outputs are a function **ONLY** of states
- Usually specified on the states.

- Mealy Model


- Named after G. Mealy
- Outputs are a function of inputs **AND** states
- Usually specified on the state transition arcs.

Moore and Mealy Example Diagrams

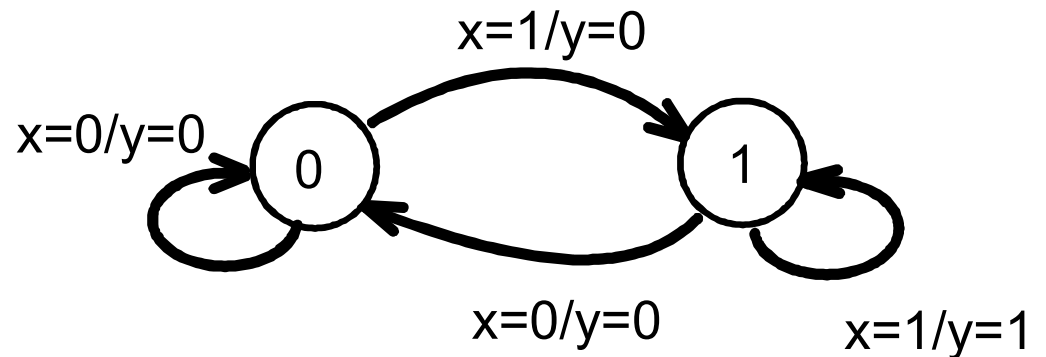- ▶ Mealy Model State Diagram maps inputs and state to outputs



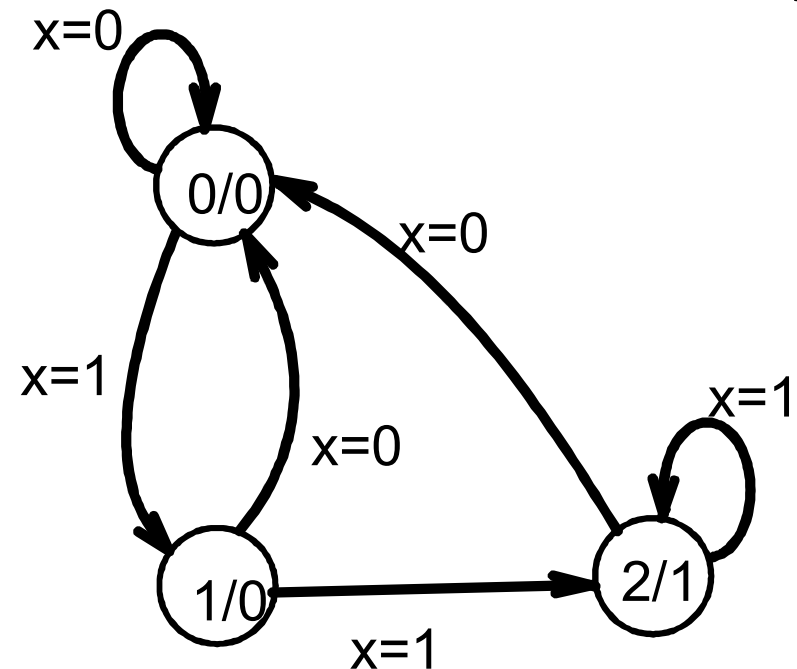- ▶ Moore Model State Diagram maps states to outputs



Moore and Mealy Example Tables

- ▶ Moore Model state table maps state to outputs

Present State	Next State		Output
	x=0	x=1	
0	0	1	0
1	0	2	0
2	0	2	1

- ▶ Mealy Model state table maps inputs and state to outputs


Present State	Next State		Output	
	x=0	x=1	x=0	x=1
0	0	1	0	0
1	0	1	0	1

Mixed Moore and Mealy Outputs

- ▶ In real designs, some outputs may be Moore type and other outputs may be Mealy type.


- ▶ Example:

- ▶ State 00: Moore
- ▶ States 01, 10, and 11: Mealy
- ▶ Simplifies output specification

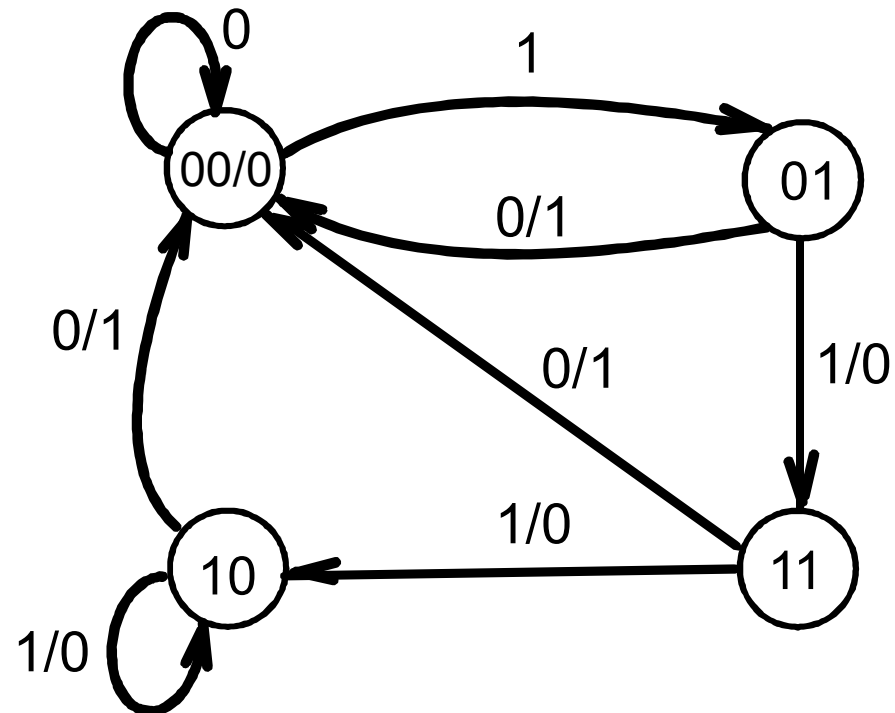

Example 2: Sequential Circuit Analysis

► Logic Diagram:

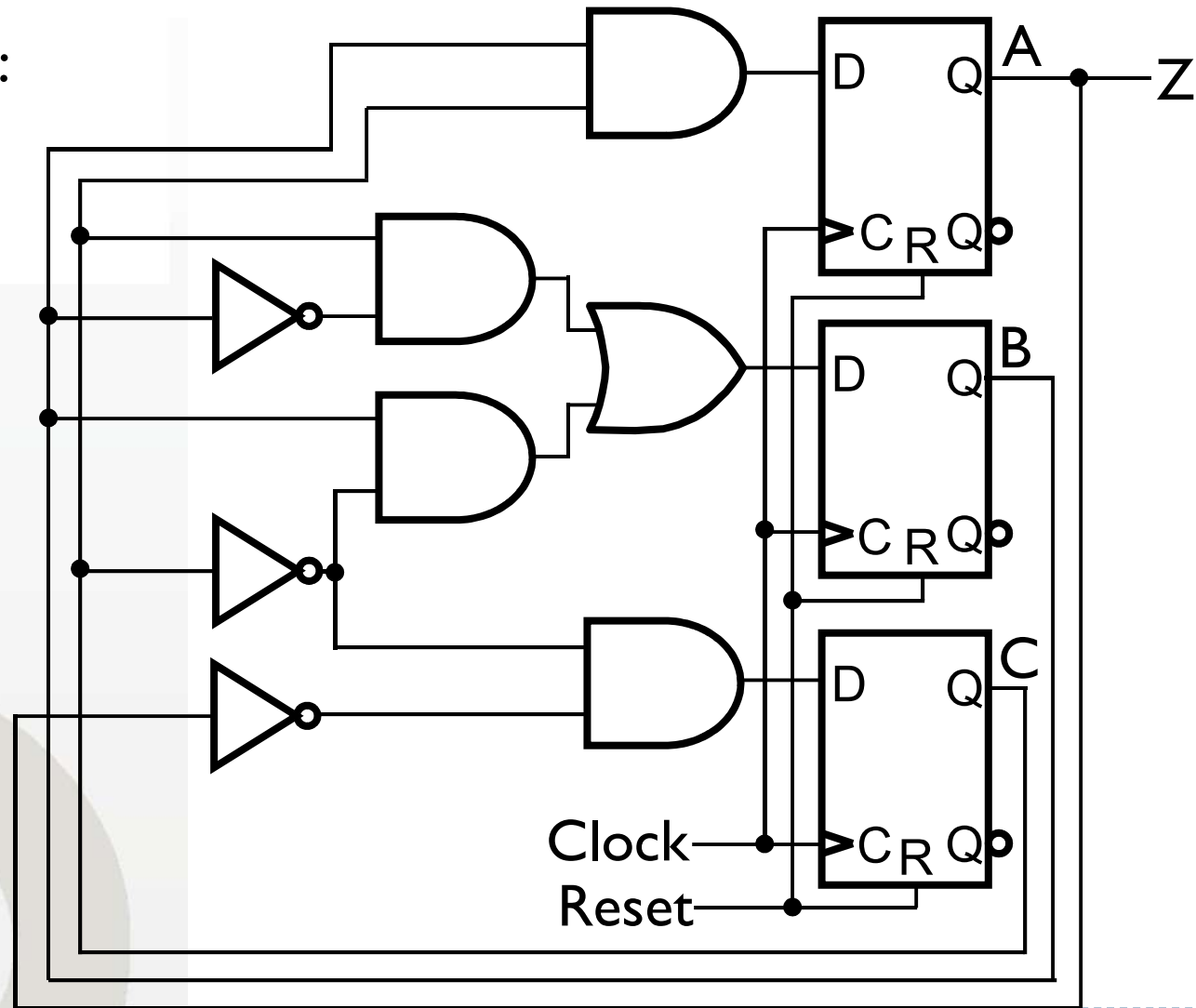

Example 2: Flip-Flop Input Equations

- ▶ Variables
 - ▶ Inputs: None
 - ▶ Outputs: Z
 - ▶ State Variables: A, B, C
- ▶ Initialization: Reset to $(0,0,0)$
- ▶ Equations
 - ▶ $A(t+1) =$
 - ▶ $B(t+1) =$
 - ▶ $C(t+1) =$


$Z =$

Example 2: State Table

$X' = X(t+1)$

A B C	A'B'C'	Z
0 0 0		
0 0 1		
0 1 0		
0 1 1		
1 0 0		
1 0 1		
1 1 0		
1 1 1		

Example 2: State Diagram

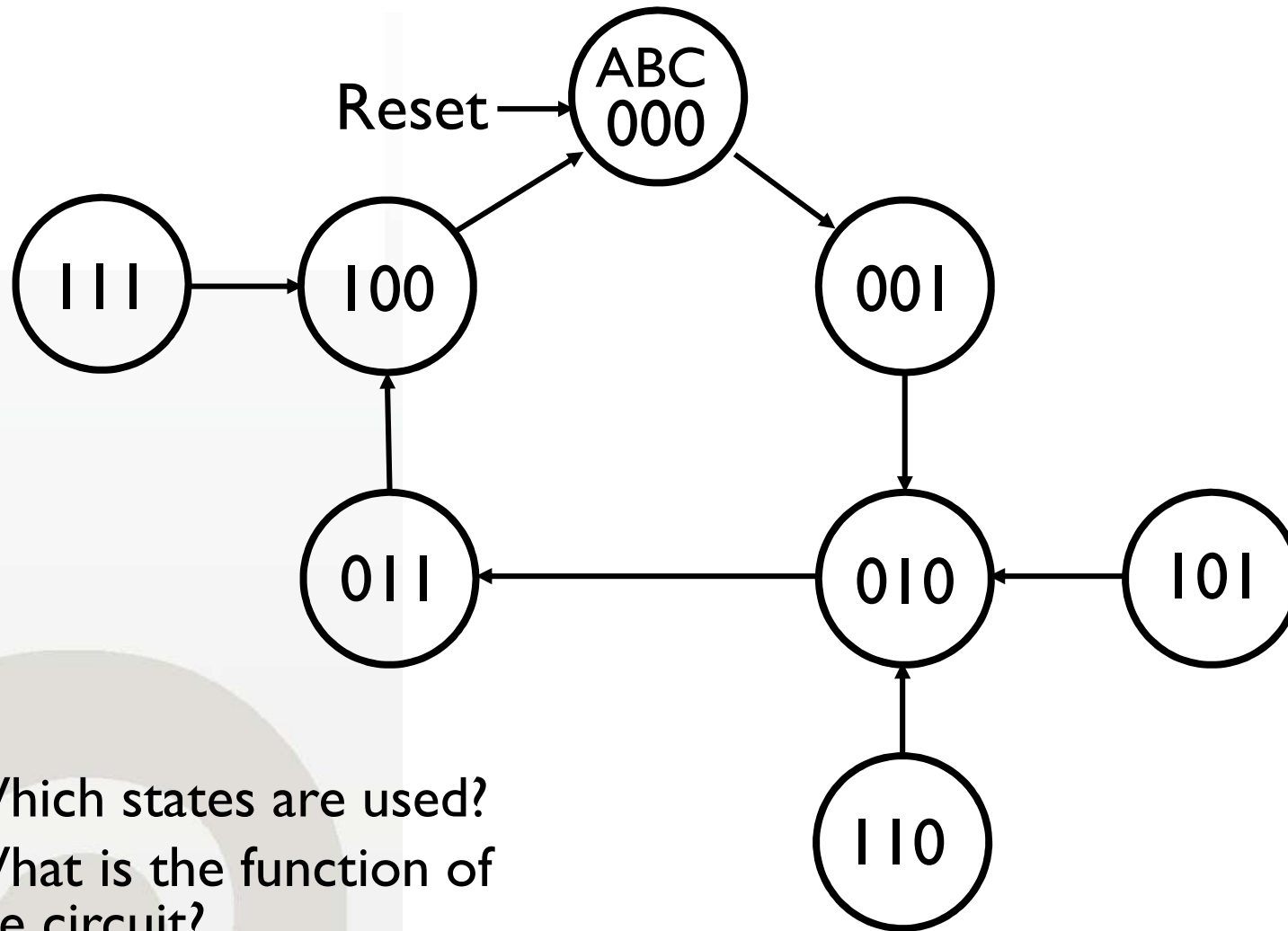

- ▶ Which states are used?
- ▶ What is the function of the circuit?

Example 3: State Diagram

A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the two following input equations:

$$A(t+1) = \bar{X}A + XY$$

$$B(t+1) = XA + \bar{X}B$$

$$Z = XB$$

- a) Draw the logic diagram of the circuit
- b) Derive the state table
- c) Derive the state diagram


Example 3: State Diagram

$$A(t+1) = \bar{X}A + XY$$

$$B(t+1) = XA + \bar{X}B$$

$$Z = XB$$

a) The logic diagram of the circuit

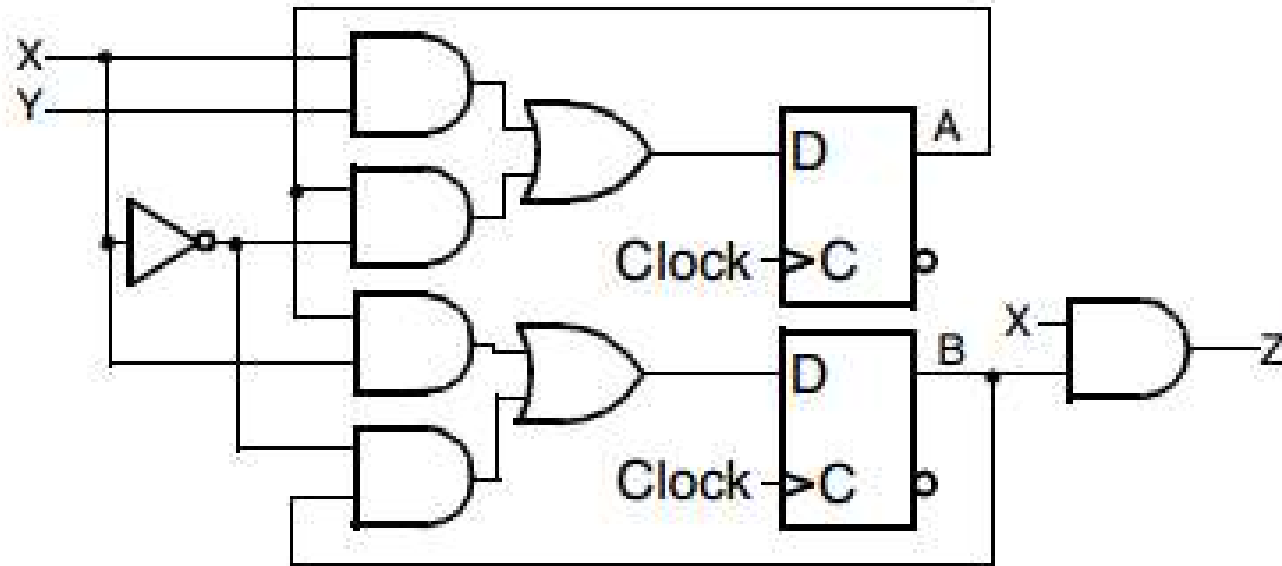

Example 3: State Diagram

$$A(t+1) = \bar{X}A + XY$$

$$B(t+1) = XA + \bar{X}B$$

$$Z = XB$$

b) The state table

Present state		Inputs		Next state		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	1	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	1	1	0
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	0	1	1
1	1	1	1	1	1	1

Example 3: State Diagram

$$A(t+1) = \bar{X}A + XY$$

$$B(t+1) = XA + \bar{X}B$$

$$Z = XB$$

c) The state diagram

S0 - 00


S1 - 01

S2 - 10

S3 - 11

Format: XY/Z (X = unspecified)

0X/0, X0/0

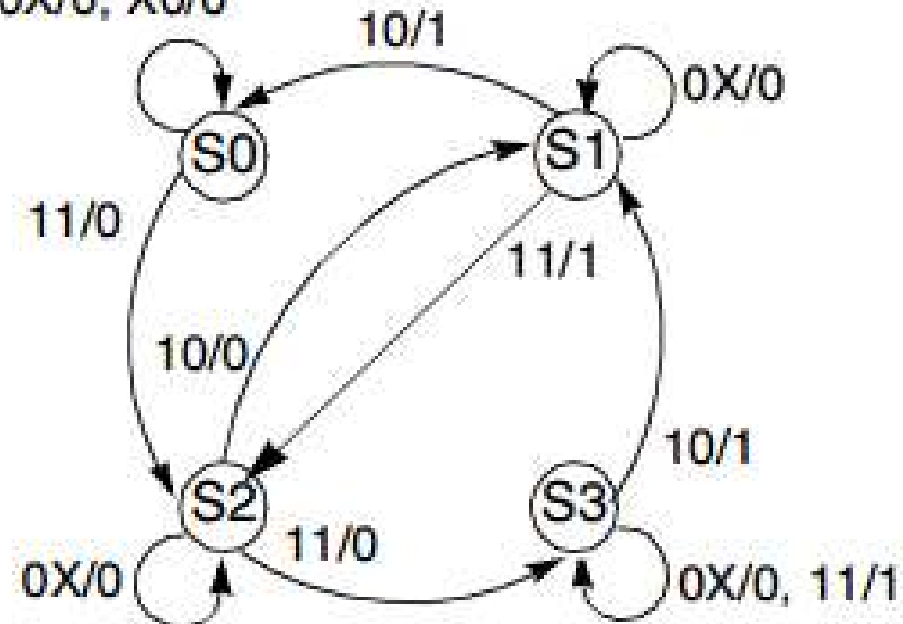

Any Questions?

