

# **ROBT206 – Microcontrollers with Lab**

## **Lecture 9 – Additional Gates and Circuits**

**6 February, 2018**

# Topics

---

## Today's Topics

Other Gate Types, NAND and NOR

Exclusive-OR Operator and Gates

High-Impedance Outputs

# Other Gate Types


---

- ▶ Basic gates are **AND, OR, NOT**.
  - ▶ Why do we need other gates?
    - ▶ Implementation feasibility and low cost
    - ▶ Power in implementing Boolean functions
    - ▶ Convenient conceptual representation
  - ▶ Gate classifications
    - ▶ Primitive gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion(s).
    - ▶ Complex gate - a gate that requires more than one primitive operation type for its description
  - ▶ Primitive gates will be covered first
-
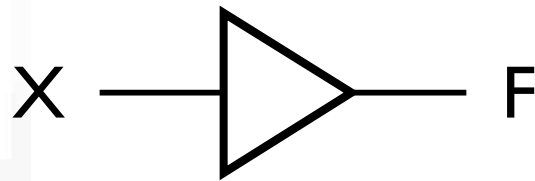
# Buffer

---

- ▶ A buffer is a gate with the function  $F = X$ :




- ▶ In terms of Boolean function, a buffer is the same as a connection!
- ▶ So why use it?
  - ▶ A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.
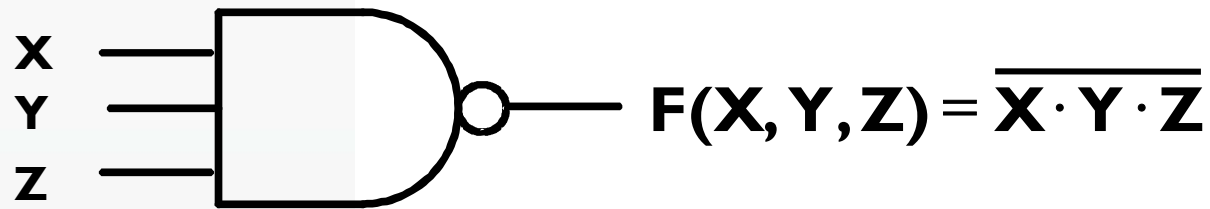
# NAND Gate

---


- ▶ The basic NAND gate has the following symbol, illustrated for three inputs:
- ▶ AND-Invert (NAND)



- ▶ NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.
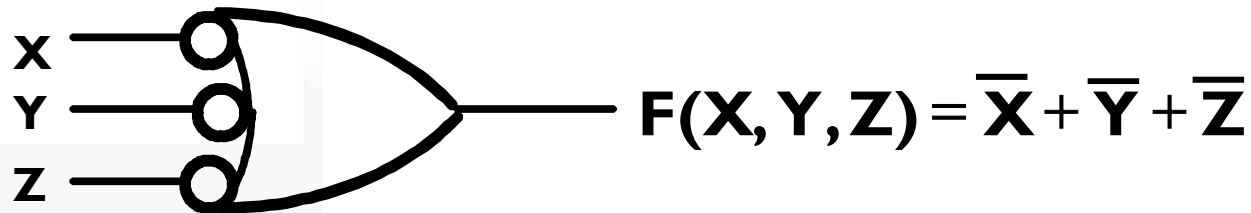
# NAND Gates

- ▶ Applying DeMorgan's Law gives Invert-OR (NAND)



- ▶ This NAND symbol is called **Invert-OR**, since inputs are inverted and then **ORed** together.
- ▶ **AND-Invert** and **Invert-OR** both represent the NAND gate. Having both makes visualization of circuit function easier.
- ▶ A NAND gate with one input degenerates to an inverter.

# NAND Gates


---

- ▶ The NAND gate is the natural implementation for CMOS (Complementary metal–oxide–semiconductor) technology in terms of chip area and speed.
  - ▶ *Universal gate* - a gate type that can implement any Boolean function.
  - ▶ NAND usually does not have a operation symbol defined since
    - ▶ the NAND operation is not associative, and
    - ▶ we have difficulty dealing with non-associative mathematics!
-

# NOR Gate

- ▶ The basic NOR gate has the following symbol, illustrated for three inputs:

- ▶ OR-Invert (NOR)

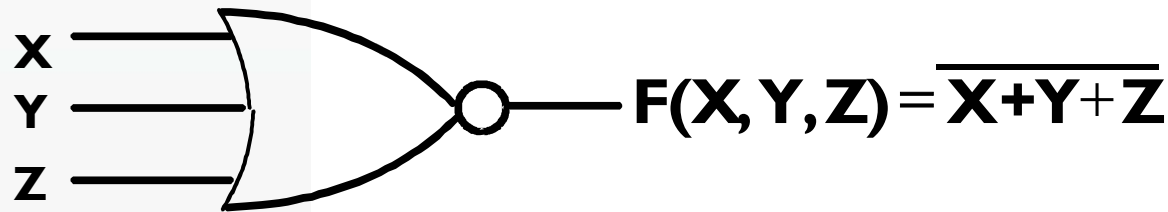


- ▶ NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert.
- ▶ The small circle (“bubble”) represents the invert function.


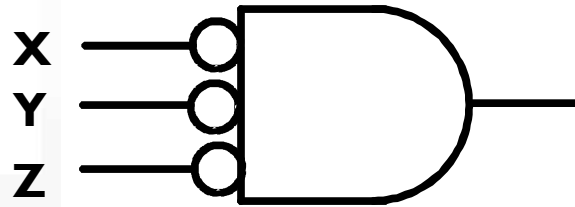
# NOR Gate

---

- ▶ Applying DeMorgan's Law gives Invert-AND (NOR)



- ▶ This NOR symbol is called Invert-AND, since inputs are inverted and then ANDed together.
- ▶ OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- ▶ A NOR gate with one input degenerates to an inverter.

# NOR Gate

---

- ▶ The NOR gate is a natural implementation for some technologies other than CMOS in terms of chip area and speed.
- ▶ The NOR gate is a universal gate
- ▶ NOR usually does not have a defined operation symbol since
  - ▶ the NOR operation is not associative, and
  - ▶ we have difficulty dealing with non-associative mathematics!

# Exclusive OR/ Exclusive NOR

---

- ▶ The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- ▶ The *eXclusive NOR* function is the complement of the XOR function

# Exclusive OR/ Exclusive NOR

- ▶ Uses for the XOR and XNORs gate include:
  - ▶ Adders/subtractors/multipliers
  - ▶ Counters/incrementers/decrementers
  - ▶ Parity generators/checkers
- ▶ Definitions
  - ▶ The XOR function is:  $\mathbf{X \oplus Y = X\bar{Y} + \bar{X}Y}$
  - ▶ The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is:  $\mathbf{\overline{X \oplus Y} = XY + \bar{X}\bar{Y}}$
- ▶ Strictly speaking, XOR and XNOR gates do not exist for more than two inputs. Instead, they are replaced by odd and even functions.

# Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$\overline{(X \oplus Y)}$ or $X \equiv Y$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:

**X OR Y, but NOT BOTH**

# XOR/XNOR

- ▶ The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum* (Mod 2 sum), not an XOR:

$$\mathbf{X \oplus Y \oplus Z = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ}$$

- ▶ The complement of the odd function is the even function.
- ▶ The XOR identities:

$$\mathbf{X \oplus 0 = X}$$

$$\mathbf{X \oplus X = 0}$$

$$\mathbf{X \oplus Y = Y \oplus X}$$

$$\mathbf{(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z}$$


$$\mathbf{X \oplus 1 = \bar{X}}$$

$$\mathbf{X \oplus \bar{X} = 1}$$


# Symbols For XOR and XNOR

---

- ▶ XOR symbol:

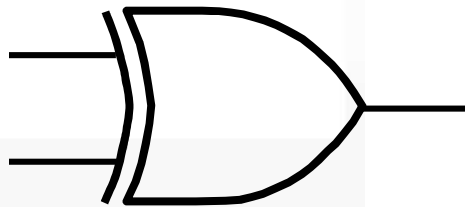


- ▶ XNOR symbol:

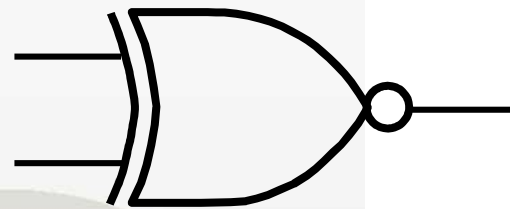


- ▶ Shaped symbols exist only for two inputs
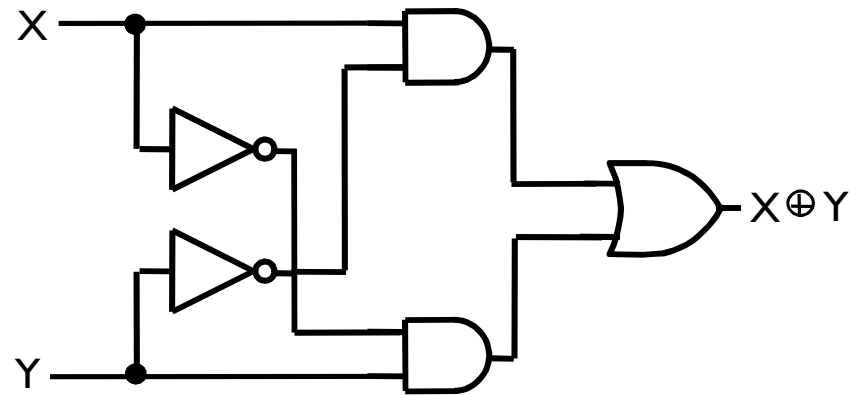
# XOR Implementations

- ▶ The simple SOP implementation uses the following structure:



- ▶ A NAND only implementation is:

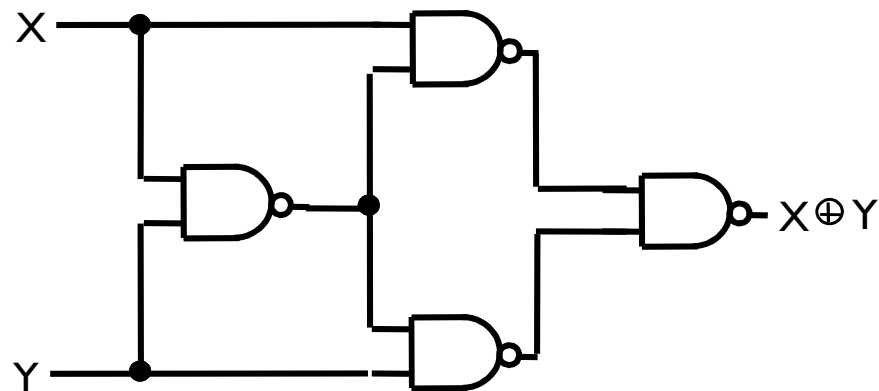



# Hi-Impedance Outputs

---

- ▶ Logic gates introduced thus far
  - ▶ have 1 and 0 output values,
  - ▶ cannot have their outputs connected together, and
  - ▶ transmit signals on connections in only one direction.
- ▶ Three-state logic adds a third logic value, Hi-Impedance (Hi-Z), giving three states: 0, 1, and Hi-Z on the outputs.


# Hi-Impedance Outputs

---

- ▶ What is a Hi-Z value?
  - ▶ The Hi-Z value behaves as an open circuit
  - ▶ This means that, looking back into the circuit, the output appears to be disconnected.
  - ▶ It is as if a switch between the internal circuitry and the output has been opened.
- ▶ Hi-Z may appear on the output of any gate, but we restrict gates to:
  - ▶ a 3-state buffer, or
  - ▶ Optional: a transmission gateeach of which has one data input and one control input.
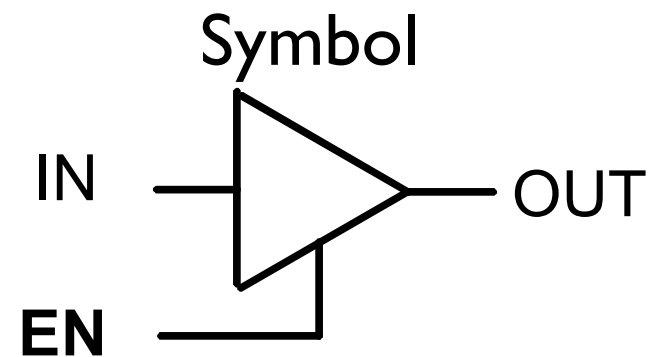
# The 3-State Buffer

- ▶ For the symbol and truth table, IN is the **data input**, and EN, the **control input**.
- ▶ For  $EN = 0$ , regardless of the value on IN (denoted by X), the output value is Hi-Z.
- ▶ For  $EN = 1$ , the output value follows the input value.
- ▶ Variations:
  - ▶ Data input, IN, can be inverted
  - ▶ Control input, EN, can be inverted by addition of “bubbles” to signals.



Truth Table

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

# Any Questions?

---

